

Всё для самостоятельного ремонта вашего автомобиля на сайте  
<http://all-audi.at.ua/> | АУДИ

РУКОВОДСТВА  
ПРОГРАММЫ  
СТАТЬИ

СОФТ ПО РЕМОНТУ АВТО.



**1996 Audi A4**

SYSTEM WIRING DIAGRAMS Audi - A4

**SYSTEM WIRING DIAGRAMS**

**Audi - A4**

**AIR CONDITIONING**

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

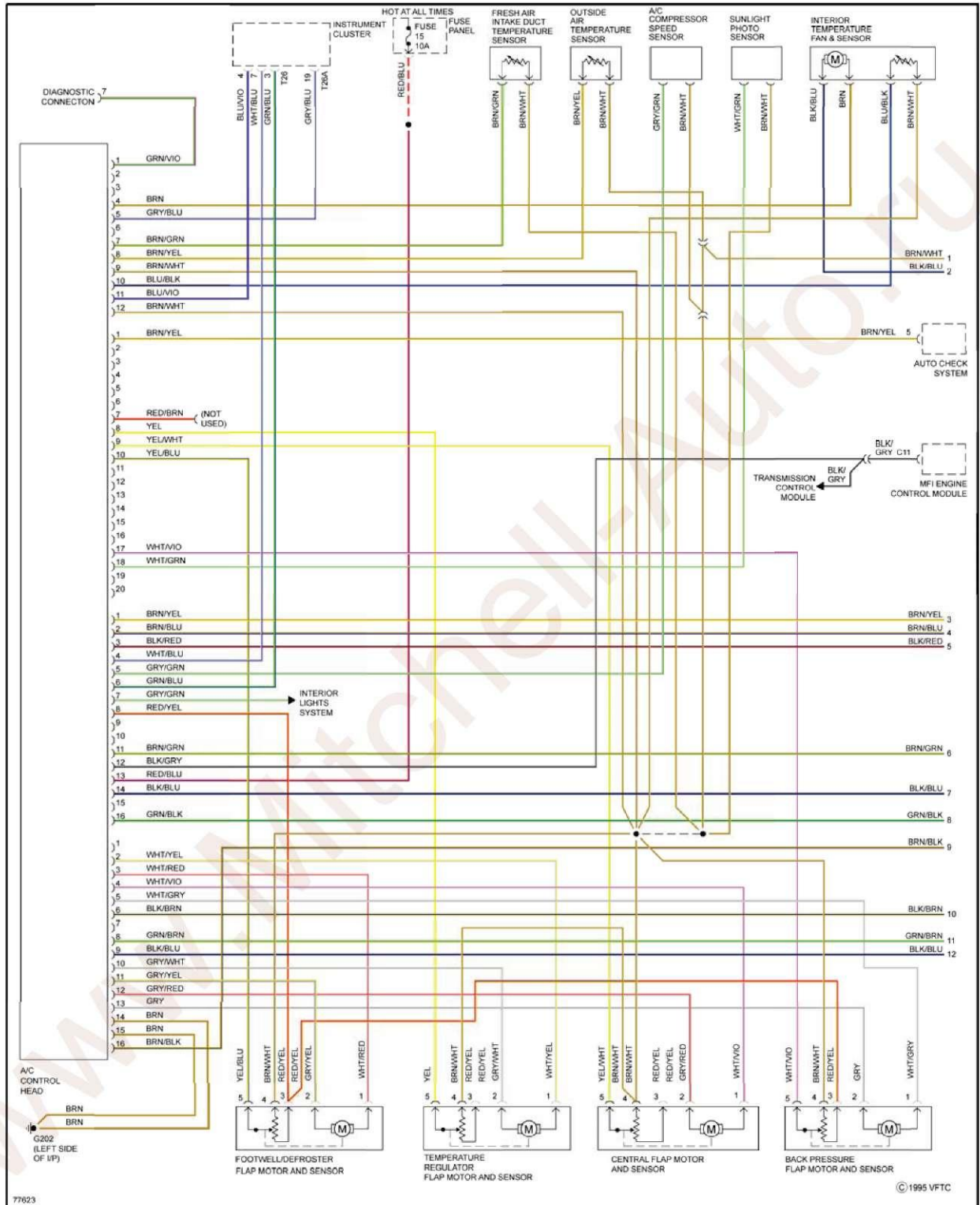


Fig. 1: Automatic A/C Circuit (1 of 2)

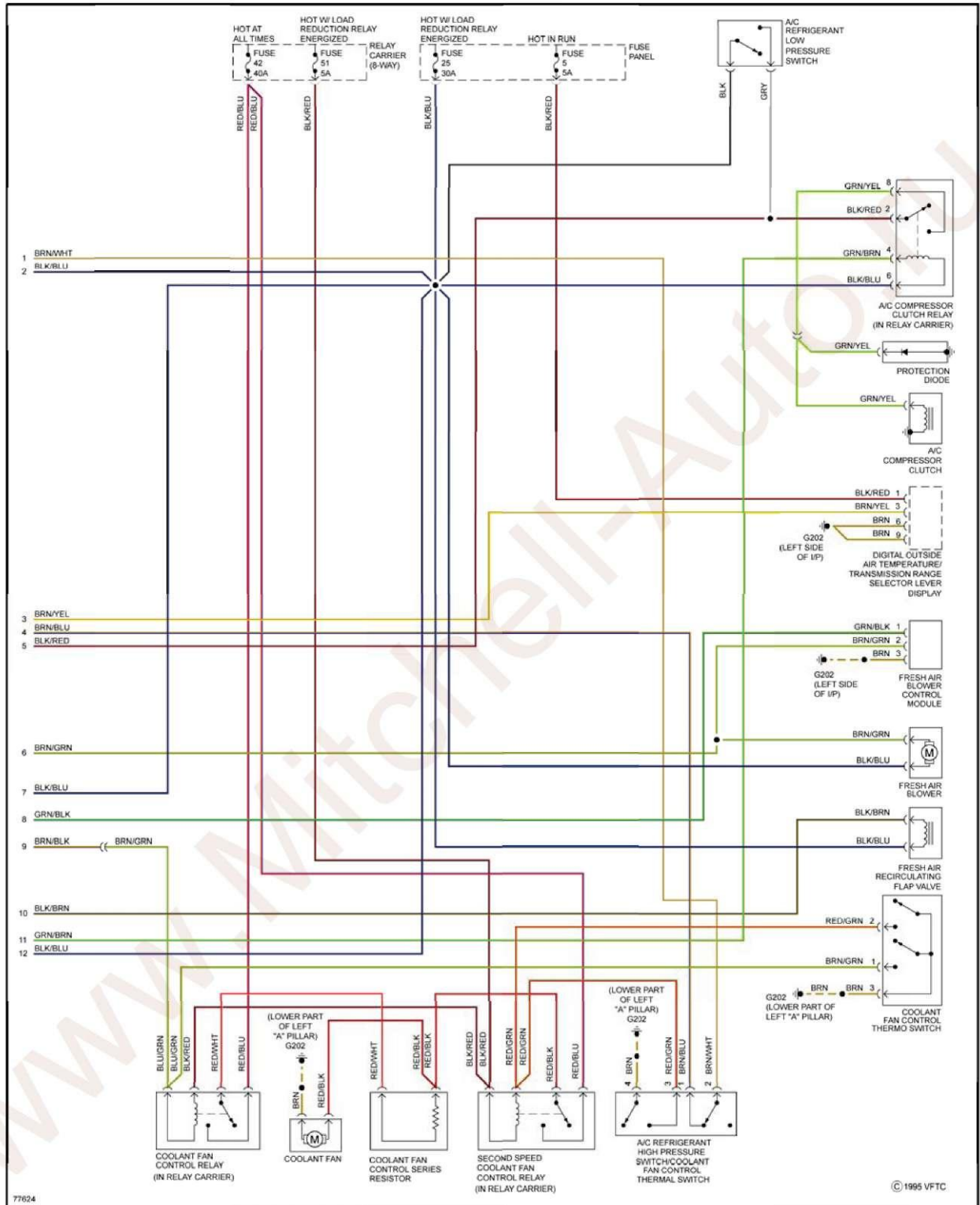



Fig. 2: Automatic A/C Circuit (2 of 2)

ANTI-LOCK BRAKES



# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

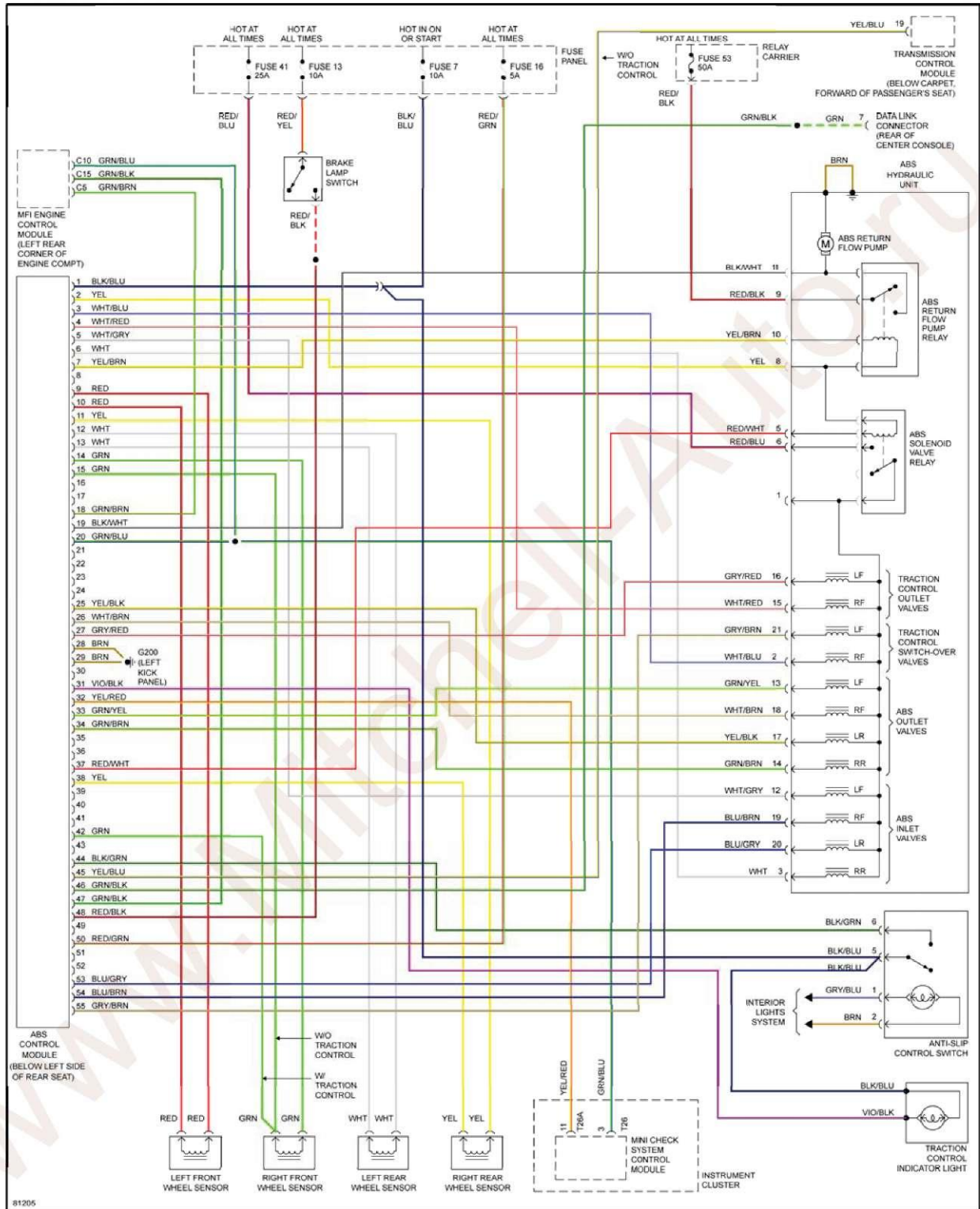

**Fig. 3: Anti-Lock Brake System Wiring Diagram (1994 S320 & S350 Circuit, FWD Without Acceleration)**

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

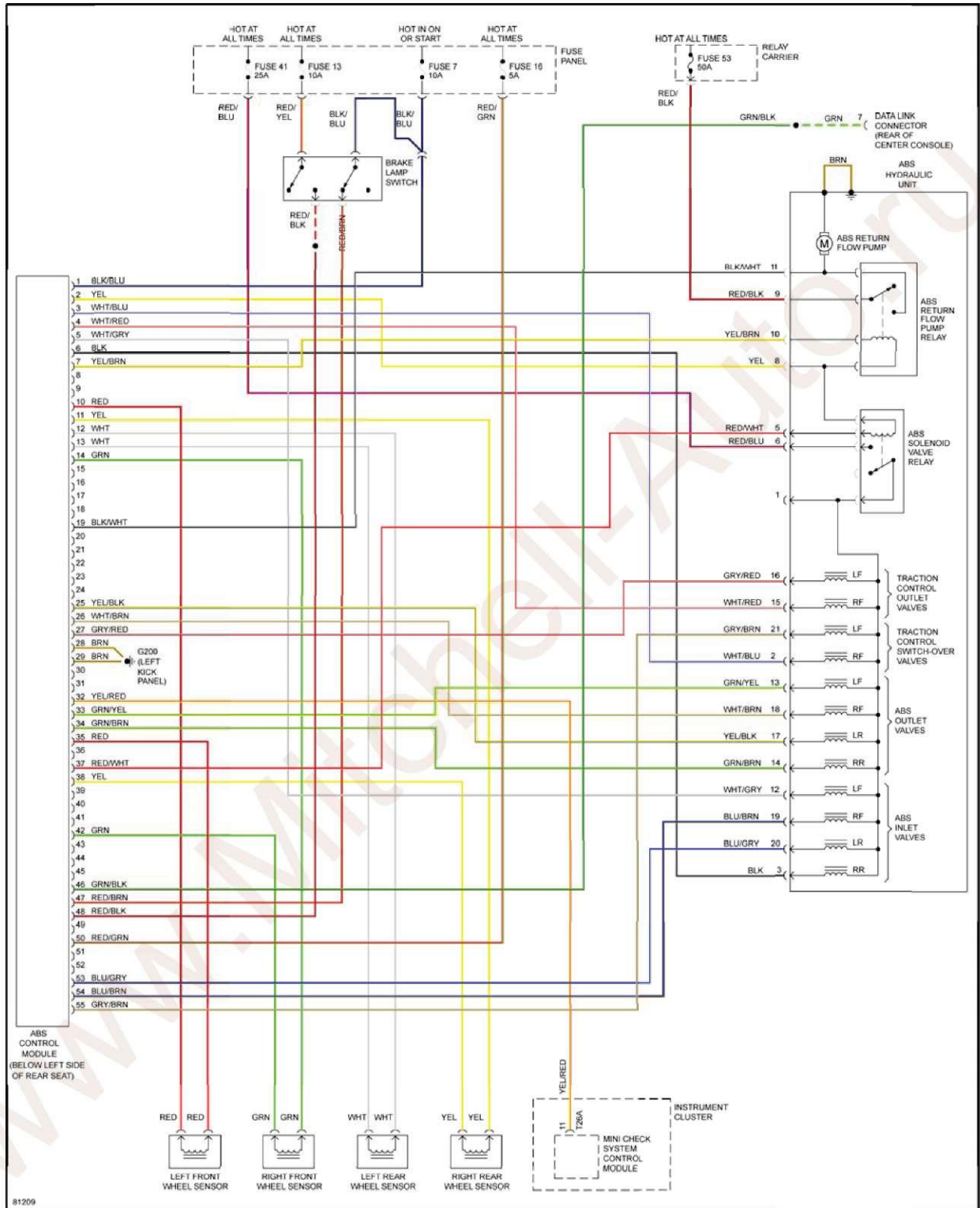


Fig. 4: Anti-lock Brakes Circuit, Quattro

### ANTI-THEFT

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

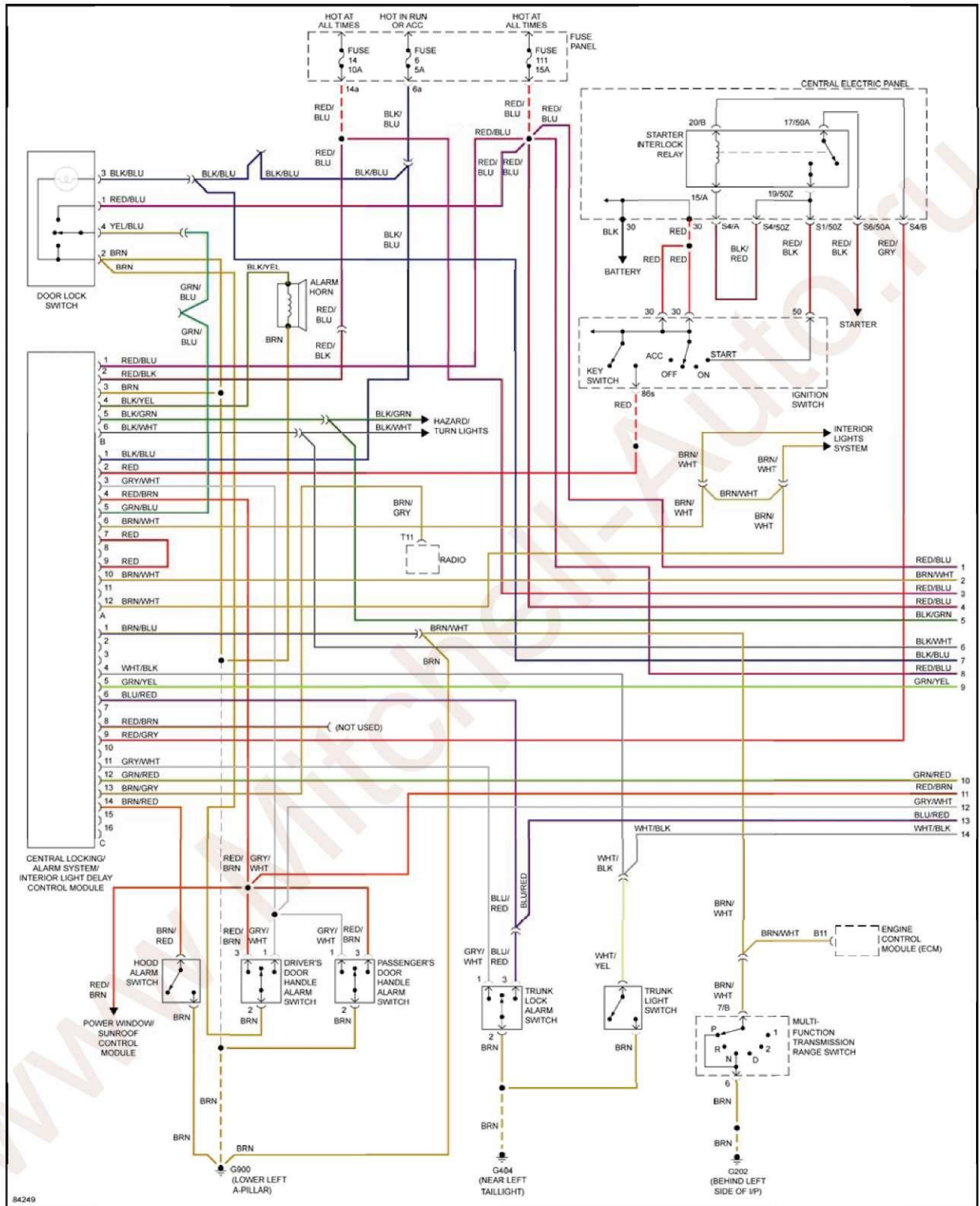


Fig. 5: Anti-theft & Central Locking Circuit (1 of 2)

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

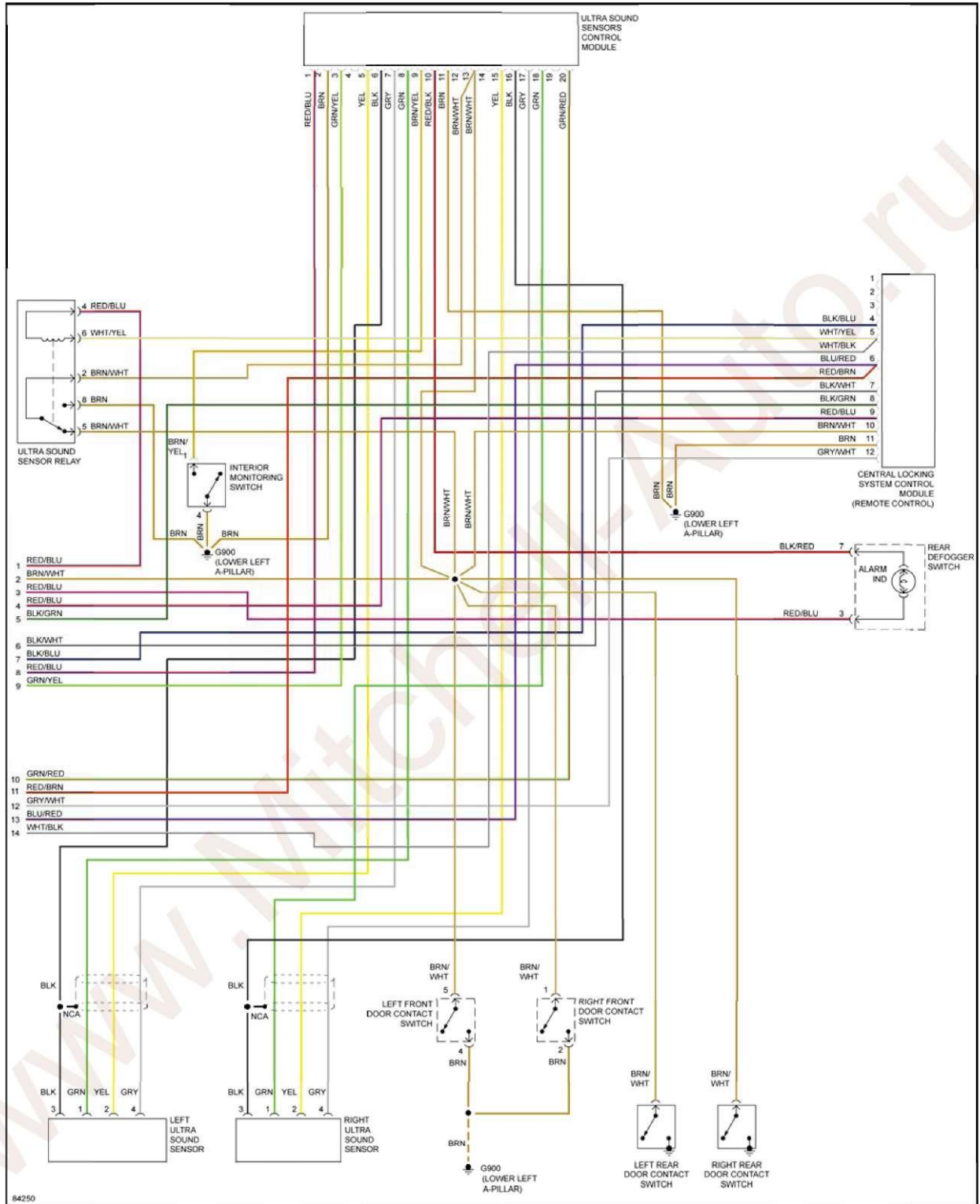


Fig. 6: Anti-theft & Central Locking Circuit (2 of 2)

## COMPUTER DATA LINES



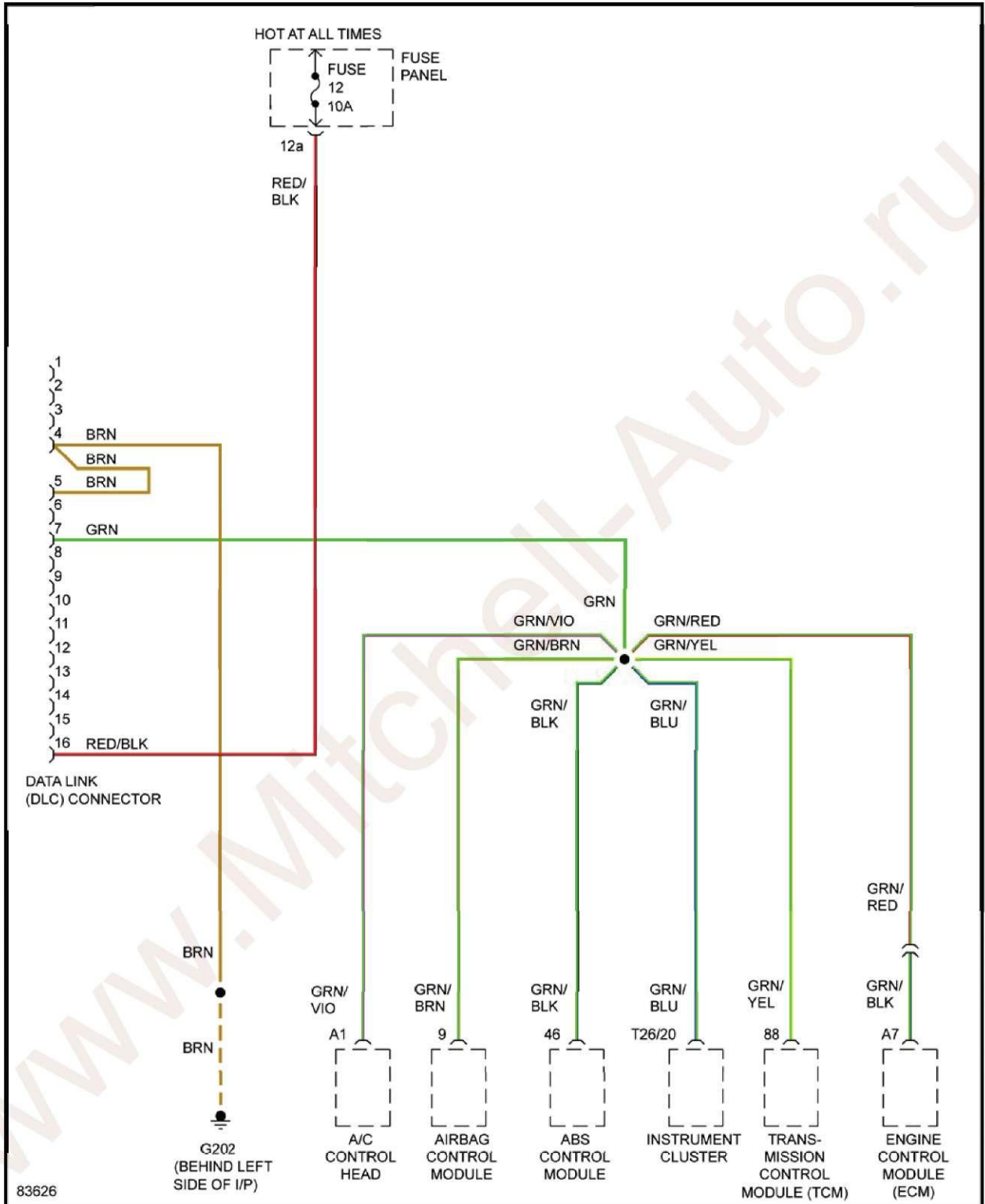


Fig. 7: Computer Data Lines Circuit

COOLING FAN

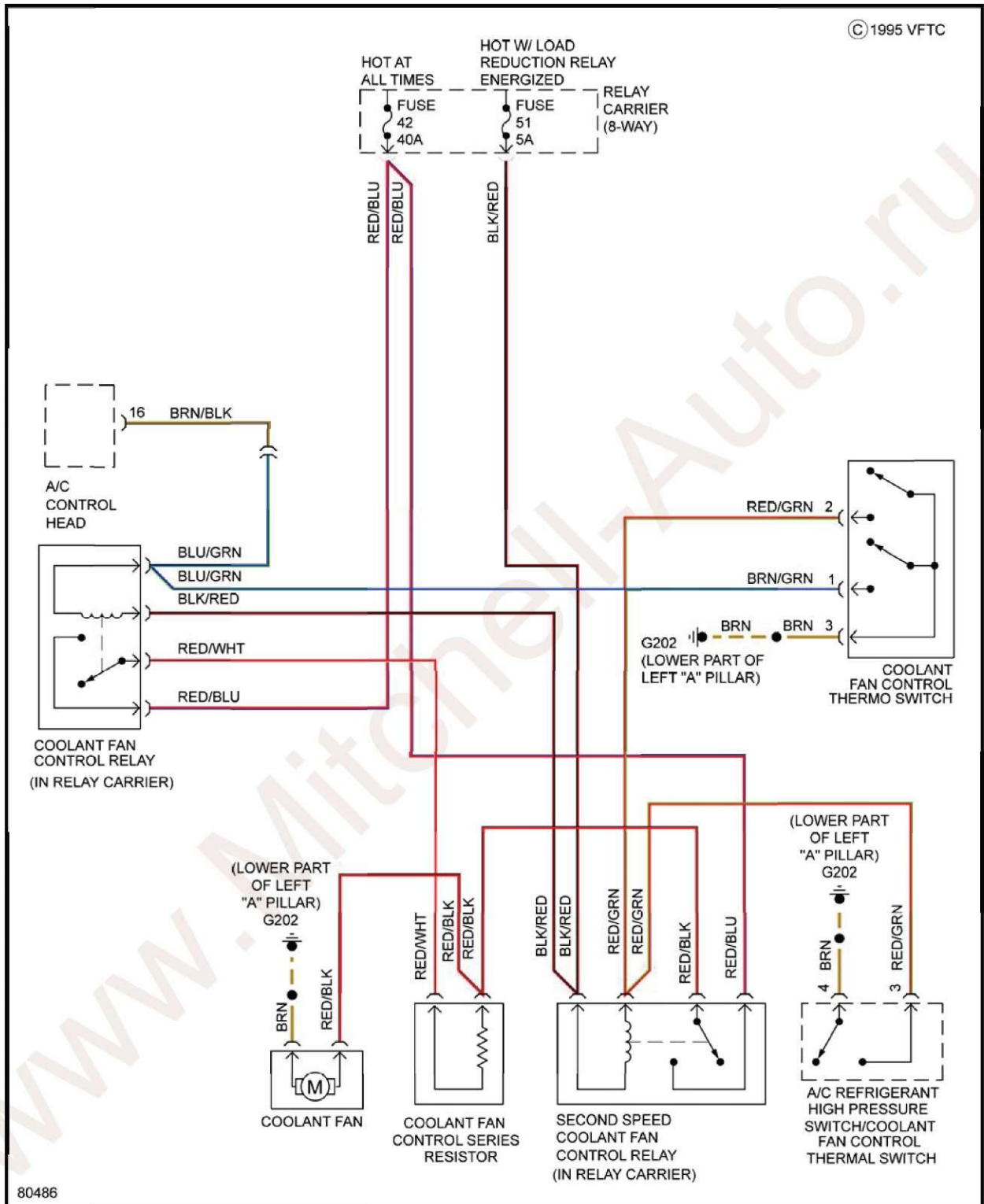


Fig. 8: Cooling Fan Circuit

CRUISE CONTROL

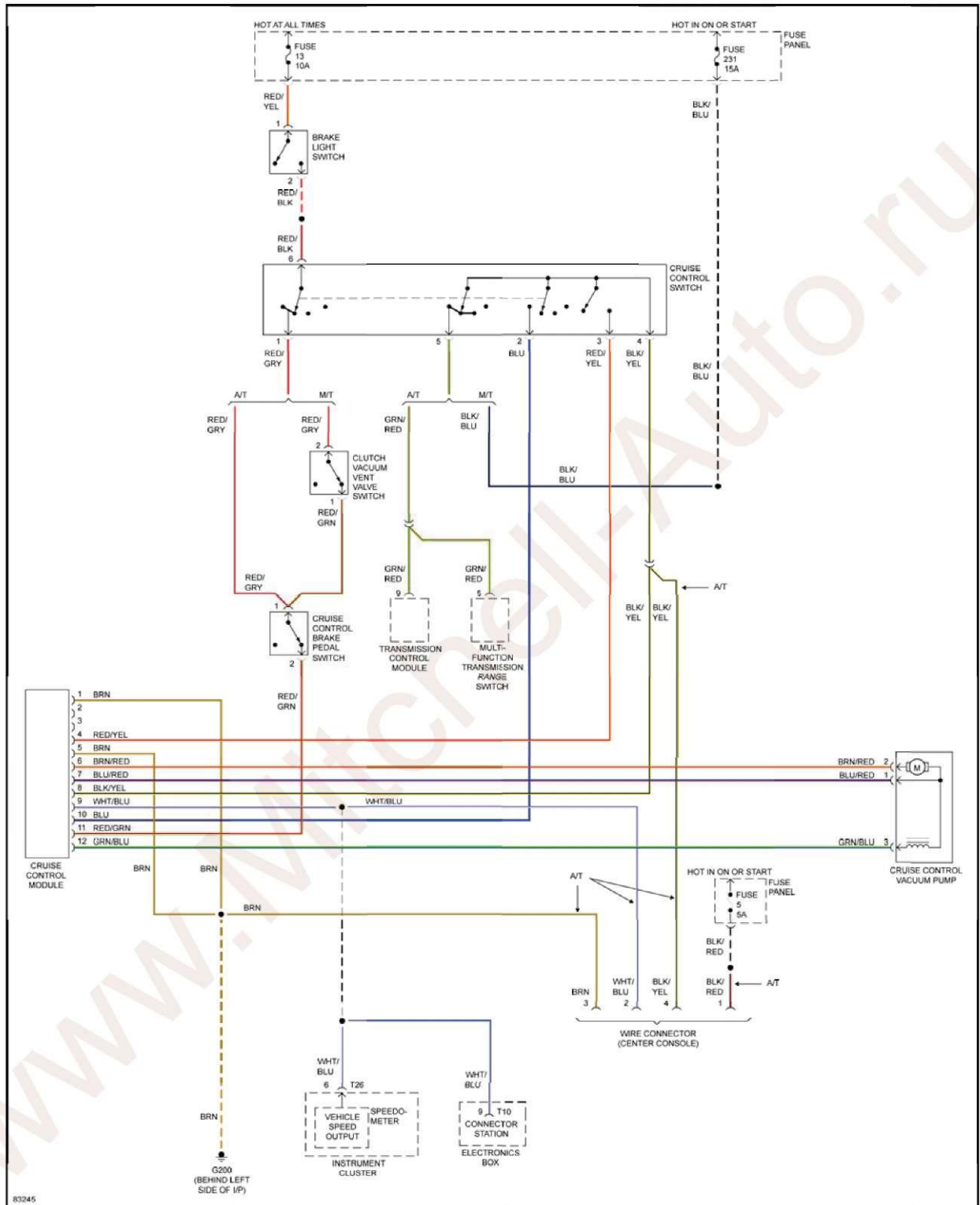


Fig. 9: Cruise Control Circuit

DEFOGGERS



# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

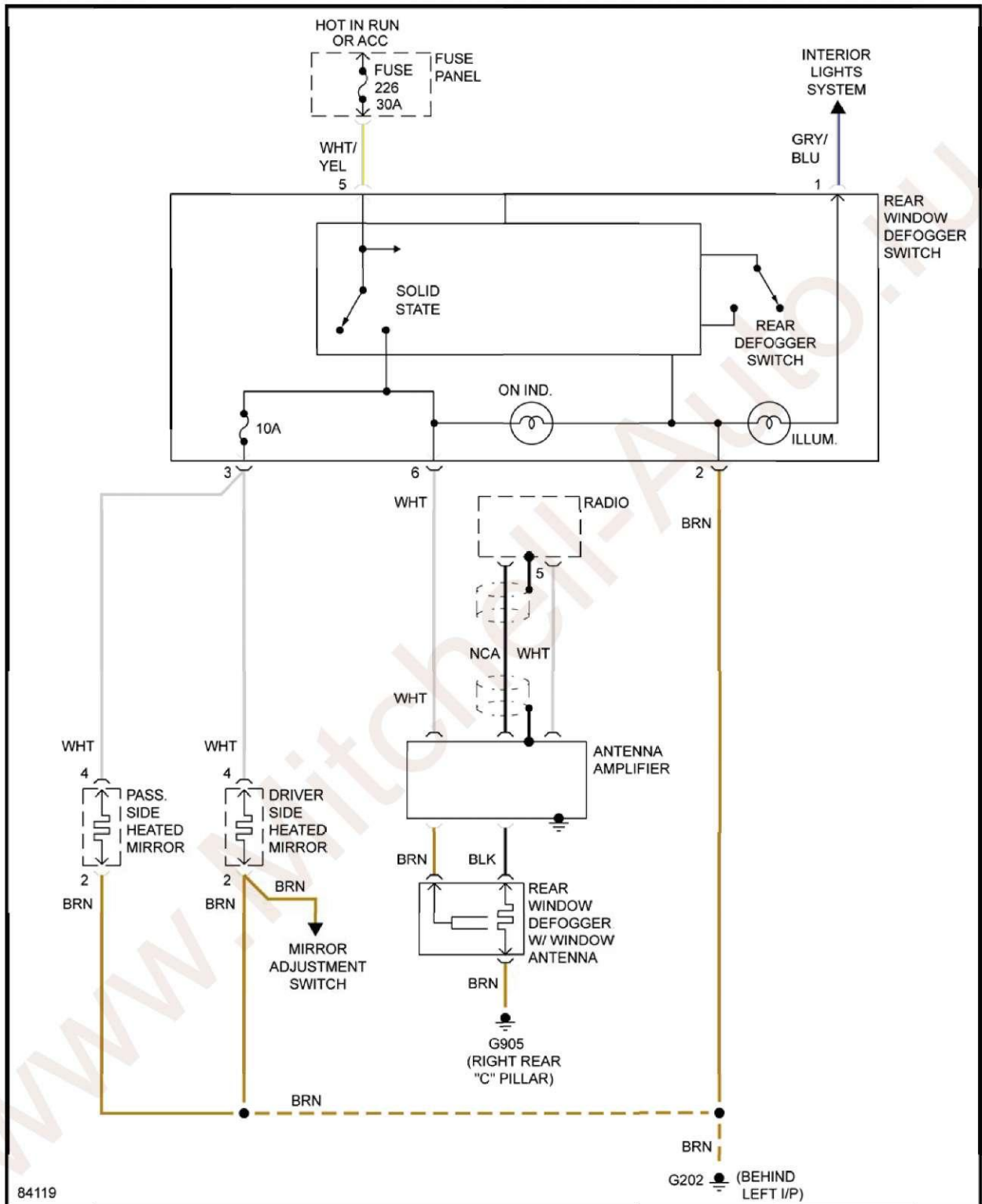


Fig. 10: W/ Antenna Amplifier Circuit

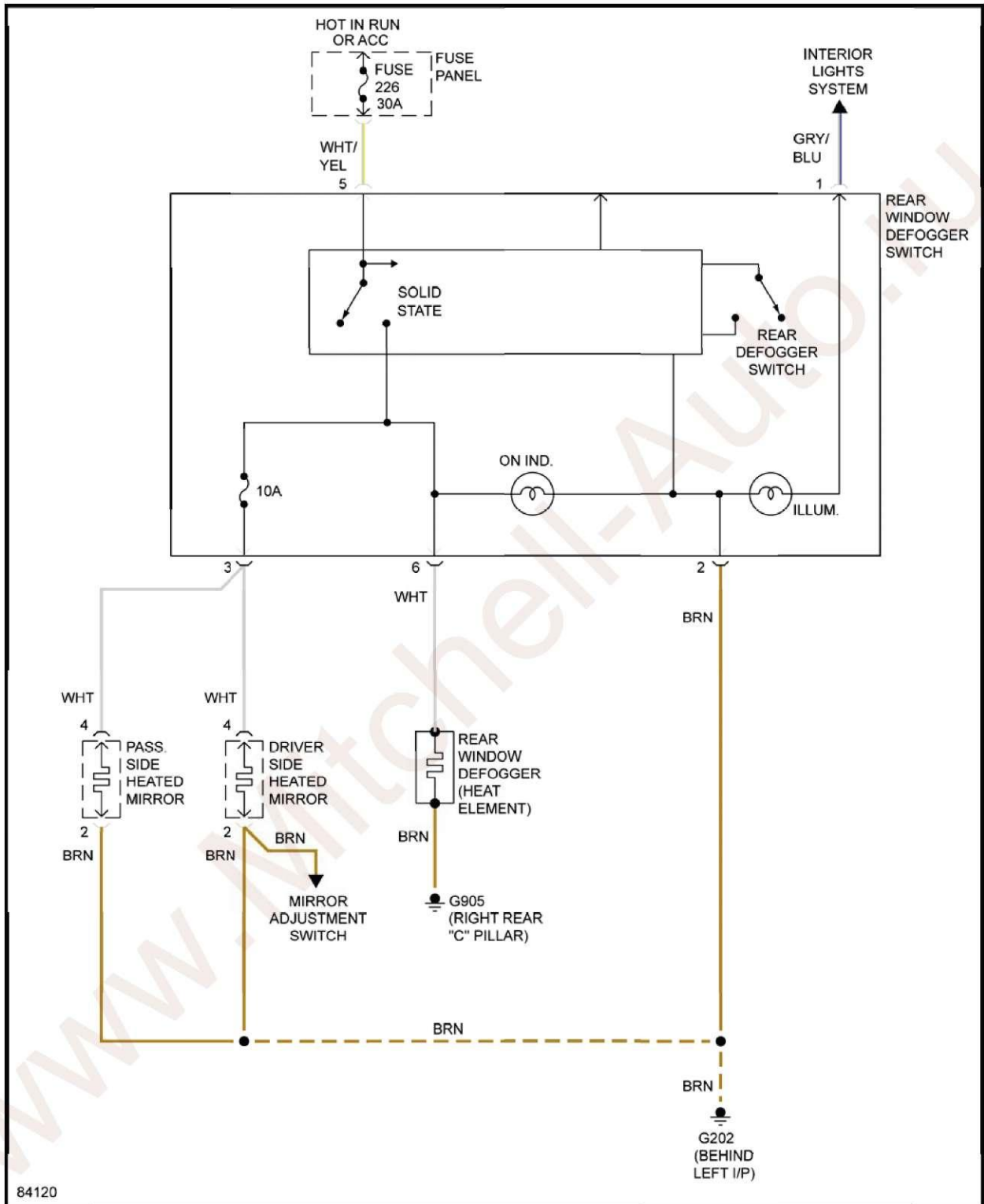


Fig. 11: W/O Antenna Amplifier Circuit

ENGINE PERFORMANCE

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

### 2.8L

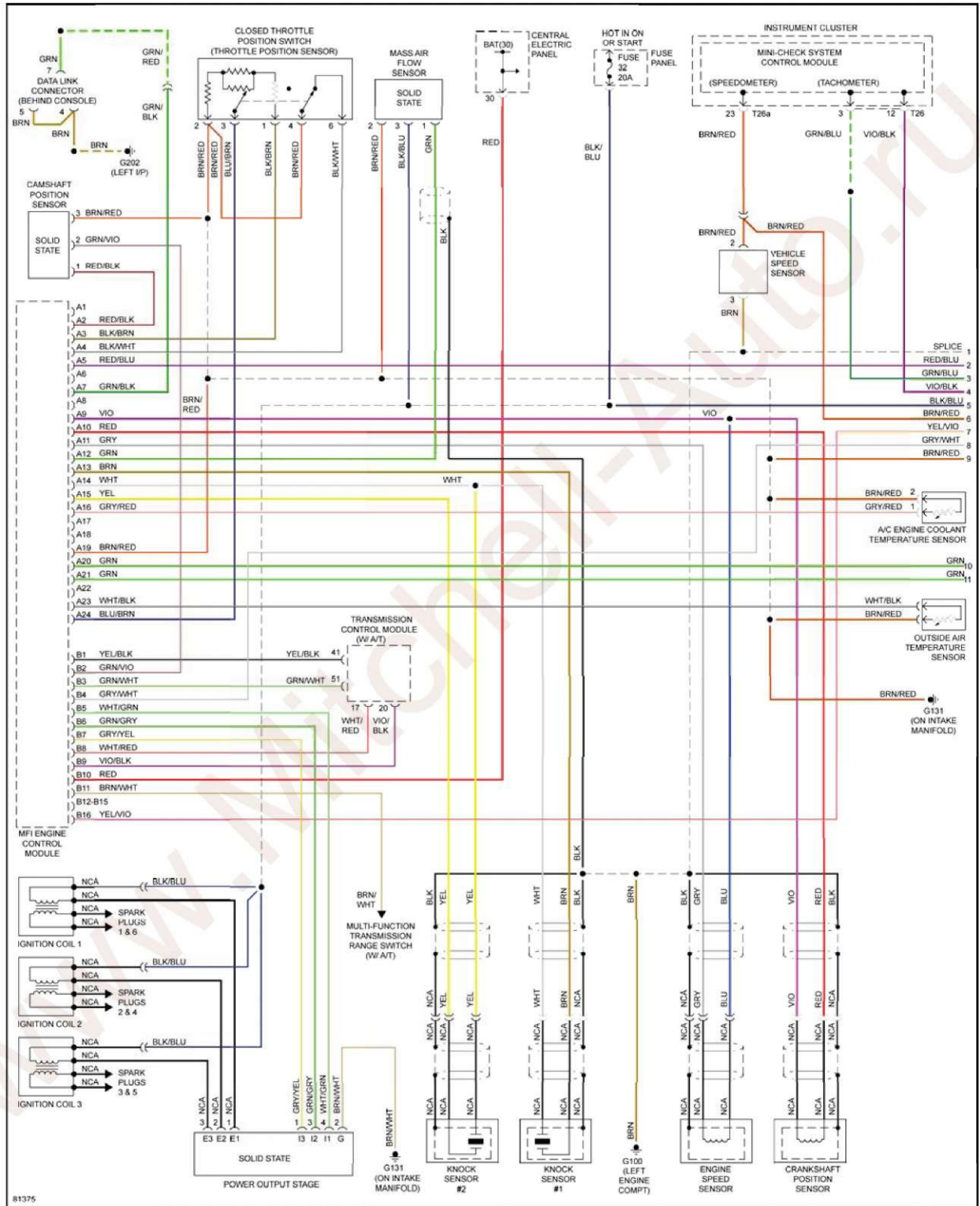


Fig. 12: 2.8L, Wiring Diagram (A4 2.8L Circuit 1 Of 2)

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

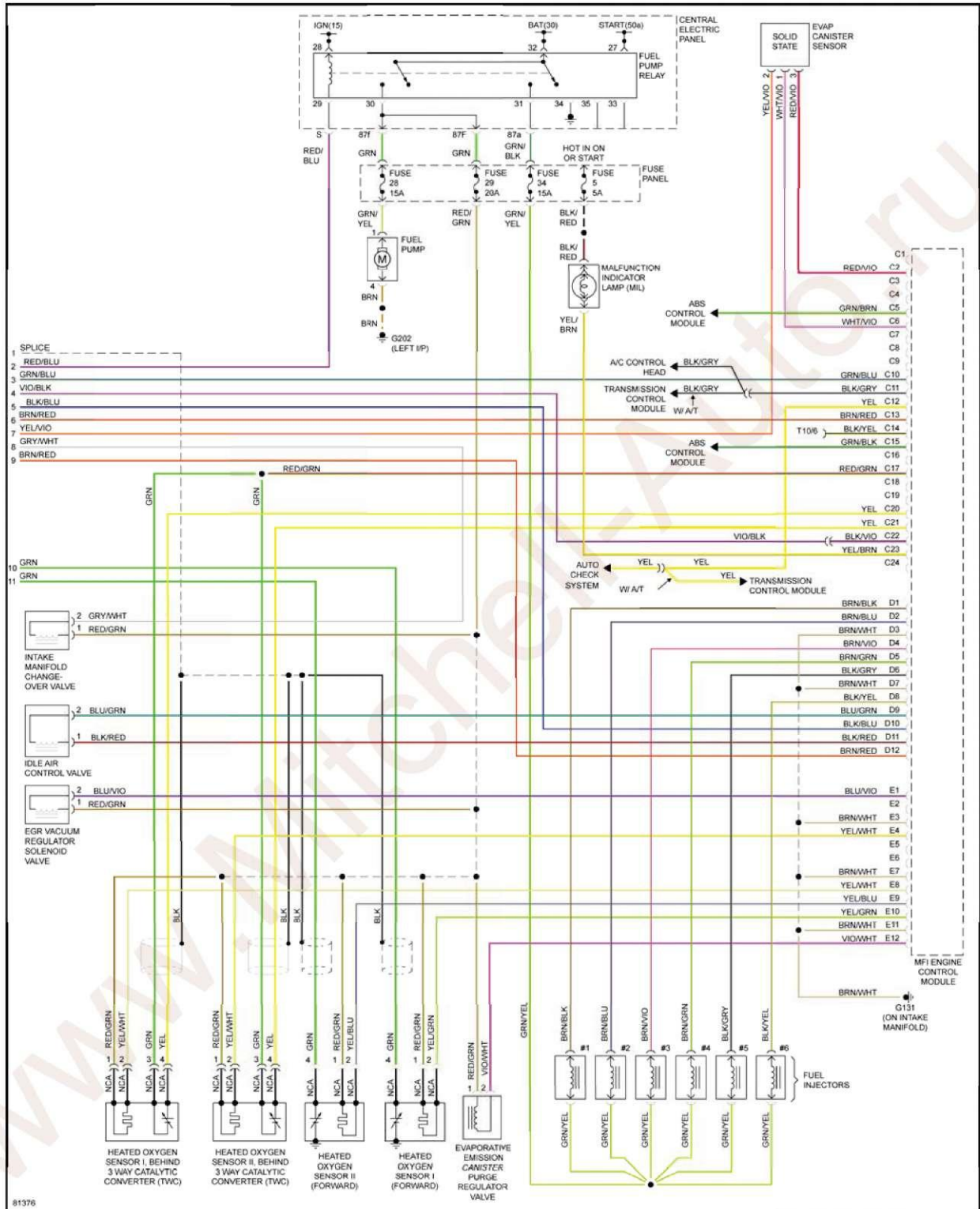


Fig. 13: 2.8L, Wiring Diagram (A4 2.8L Circuit 2 Of 2)

### EXTERIOR LIGHTS

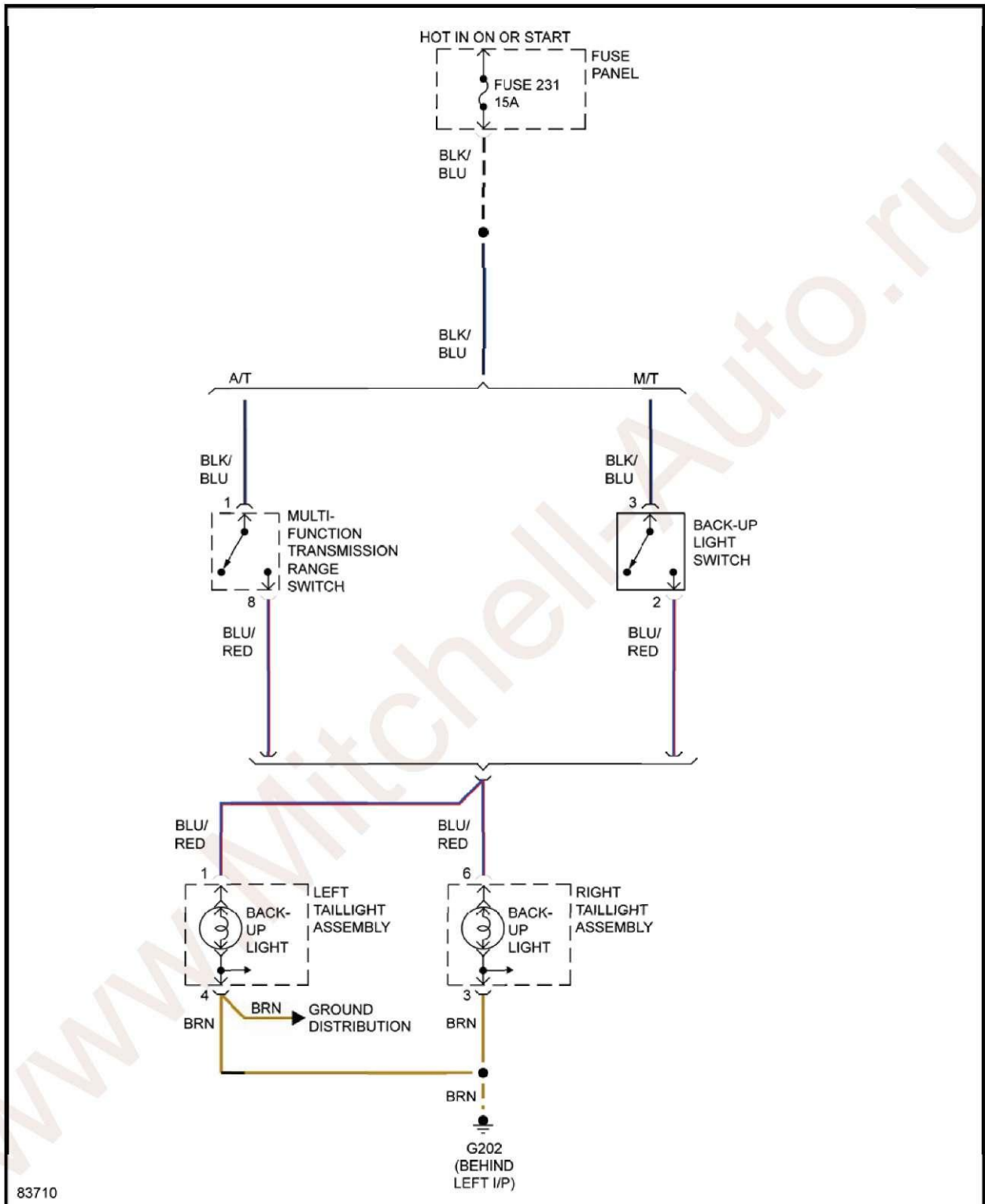


Fig. 14: Back-up Lamps Circuit



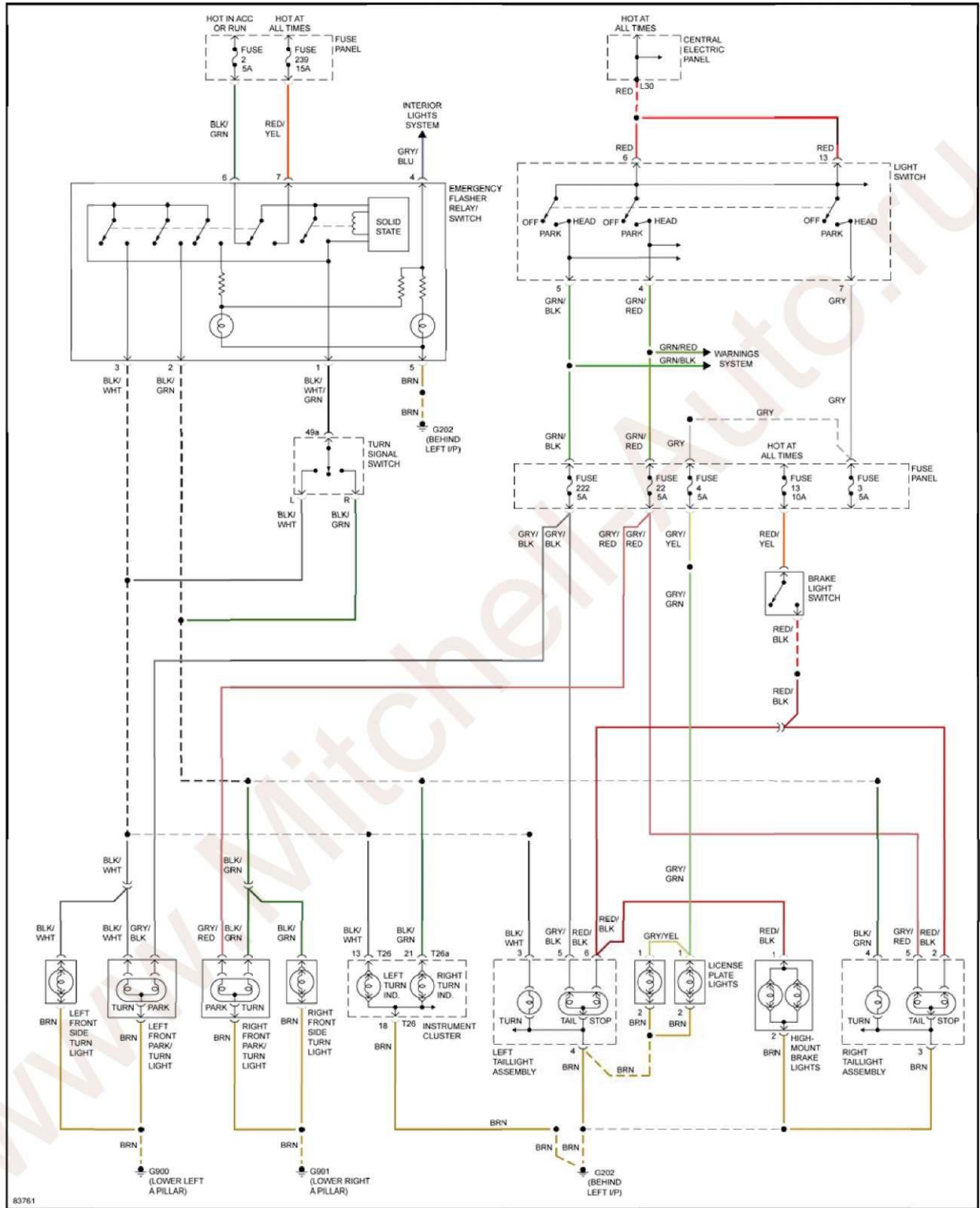


Fig. 15: Exterior Lamps Circuit

GROUND DISTRIBUTION

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

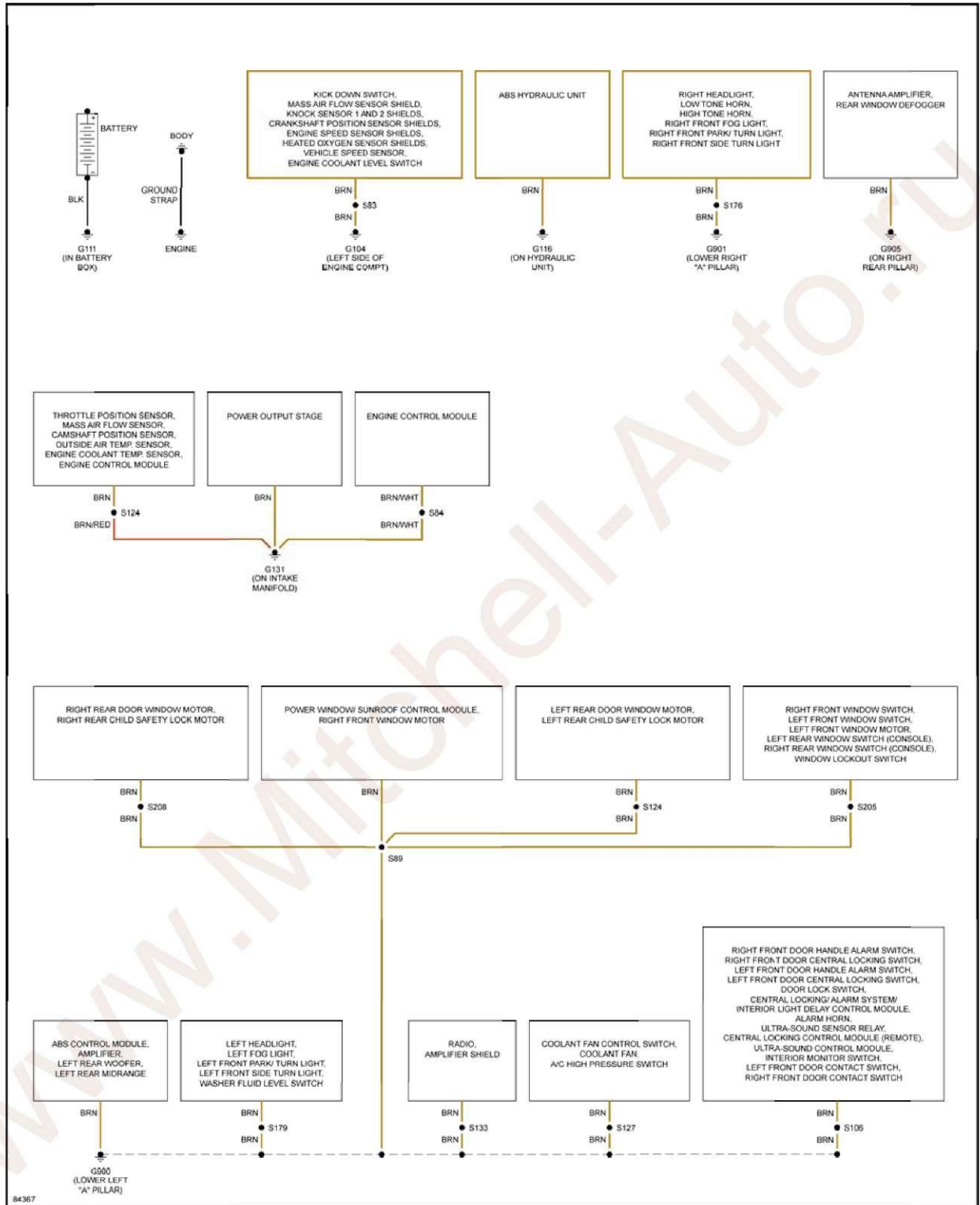


Fig. 16: Ground Distribution Circuit (1 of 2)



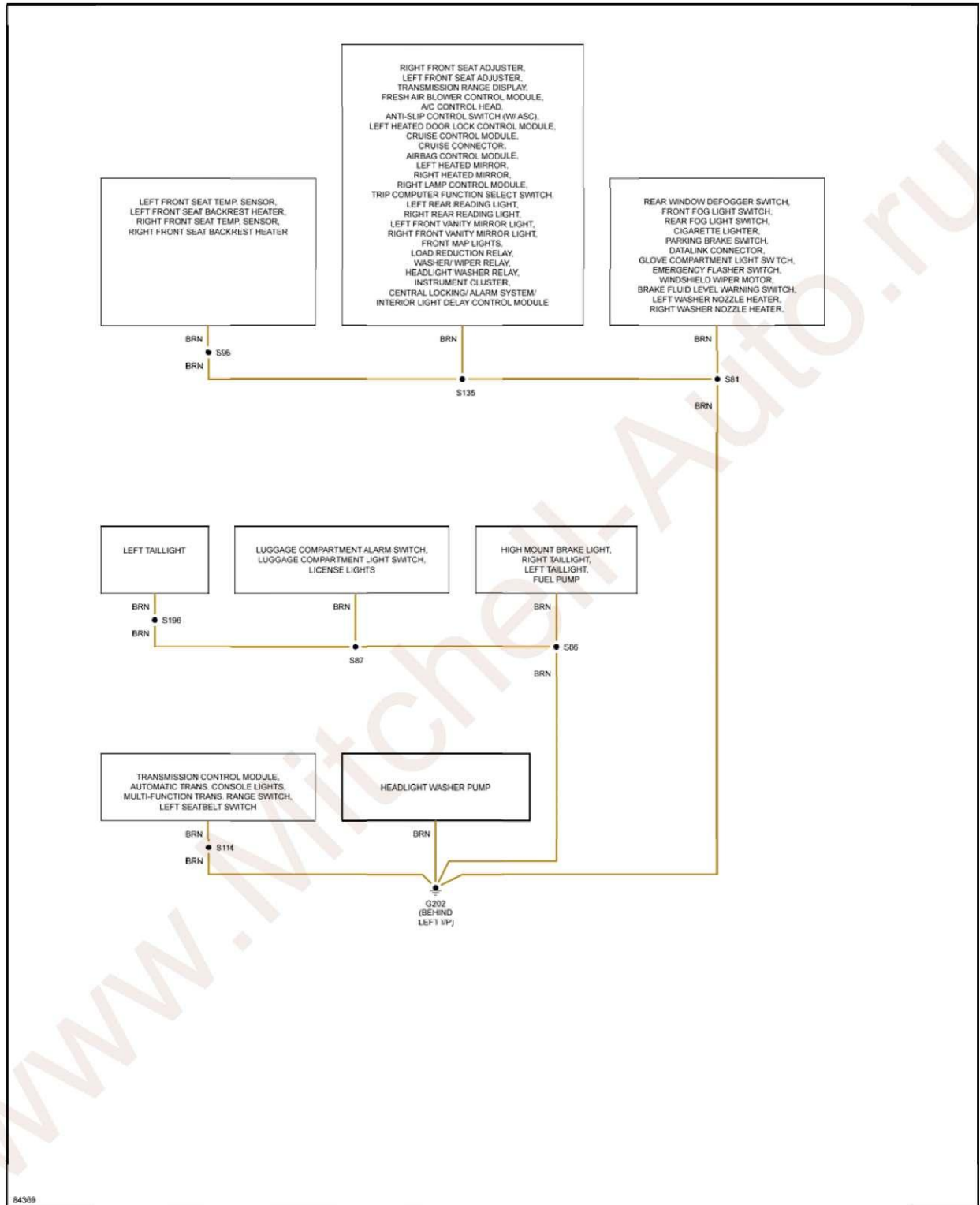


Fig. 17: Ground Distribution Circuit (2 of 2)

HEADLIGHTS

1996 Audi A4

SYSTEM WIRING DIAGRAMS Audi - A4

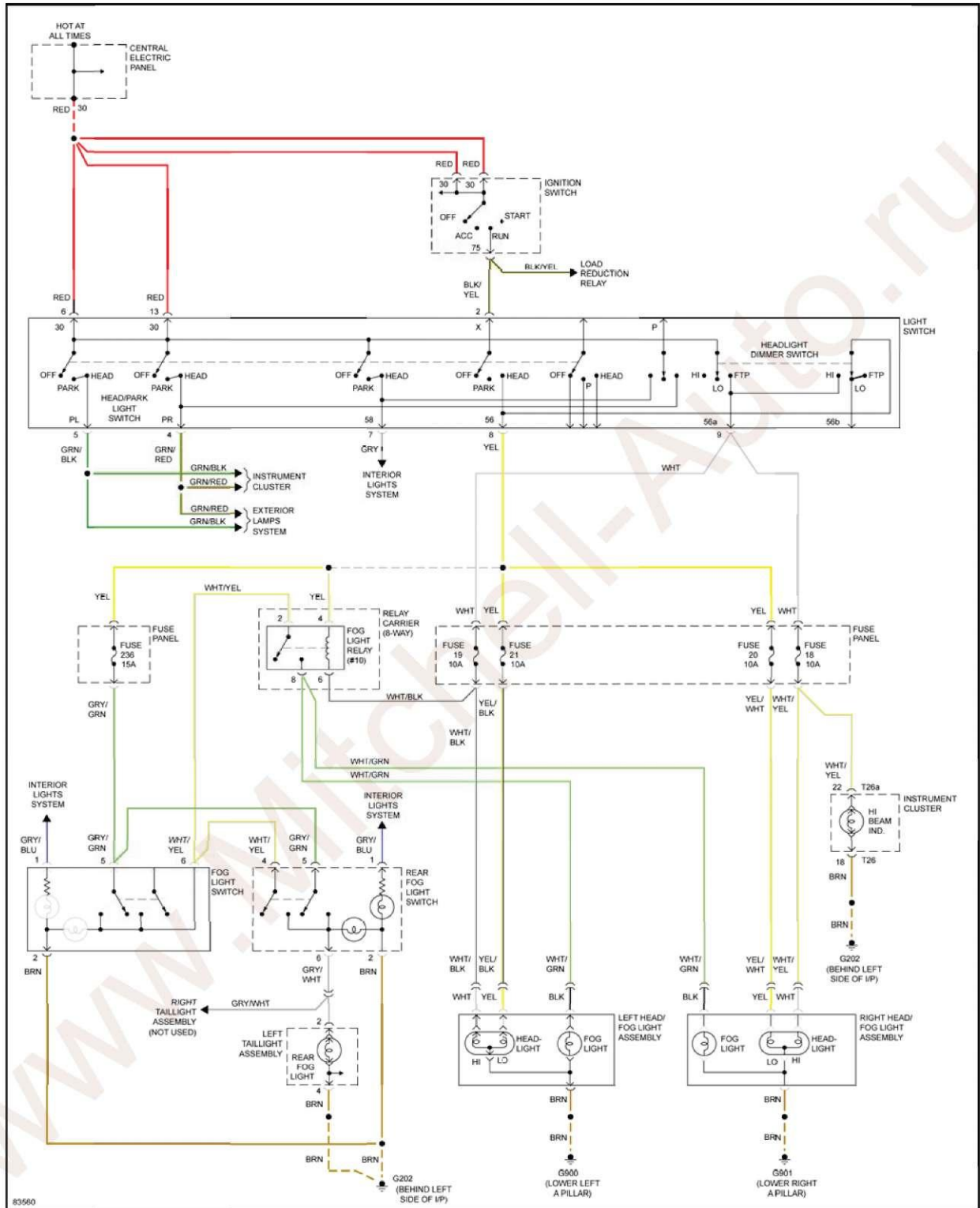


Fig. 18: Headlights Circuit

HORN


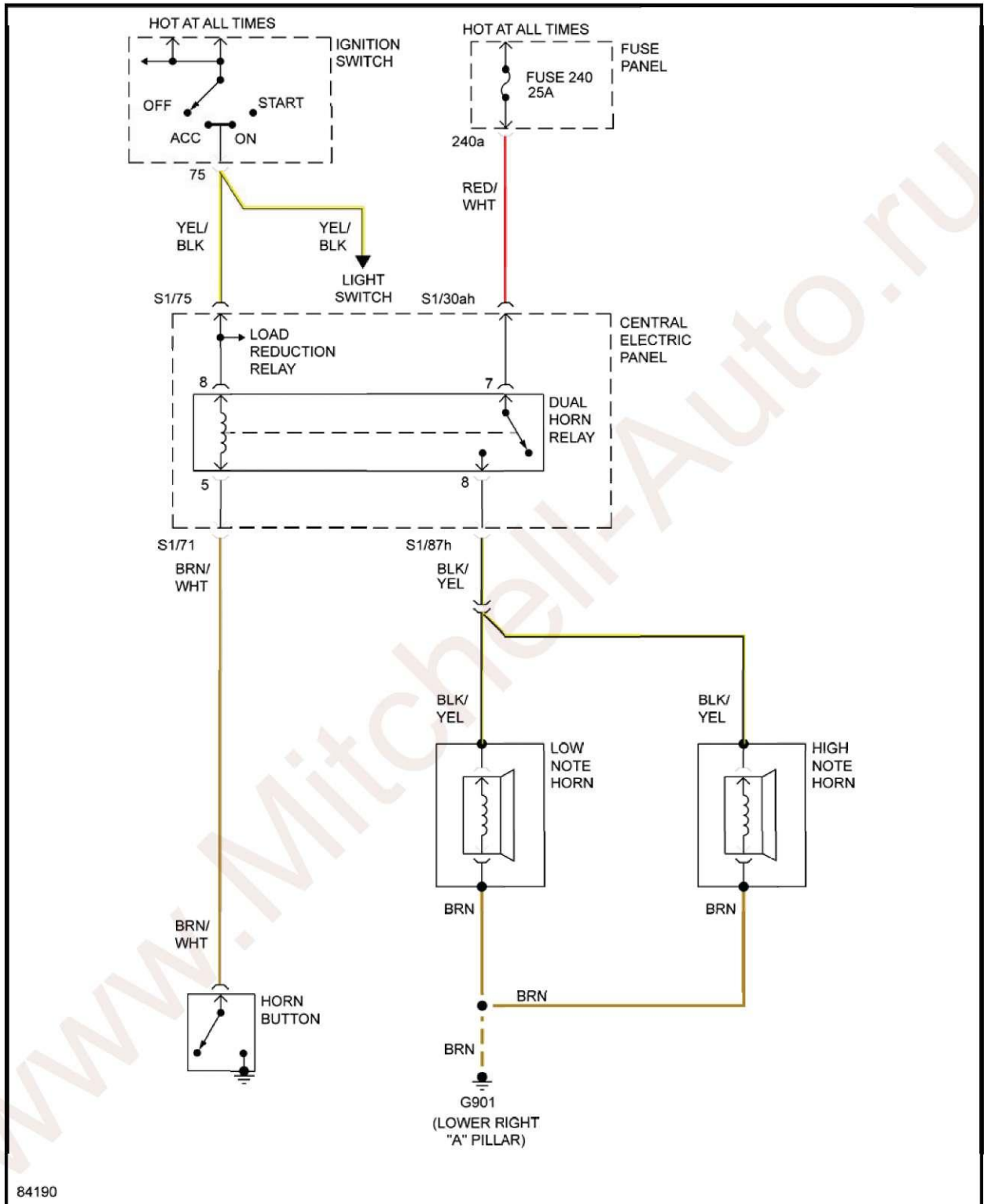


Fig. 19: Horn Circuit

INSTRUMENT CLUSTER

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

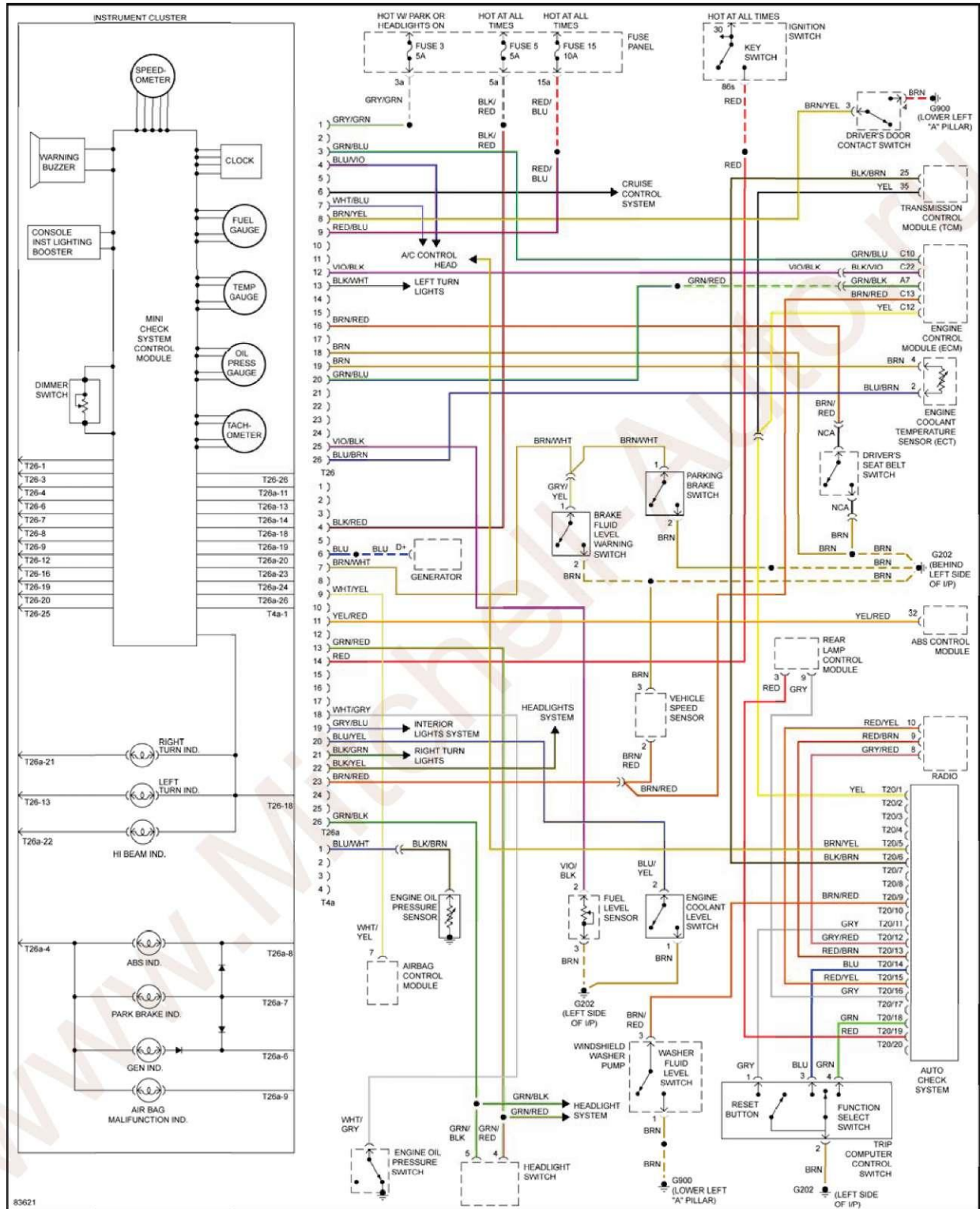

**Fig. 20: Instrument Cluster Circuit**

## INTERIOR LIGHTS

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

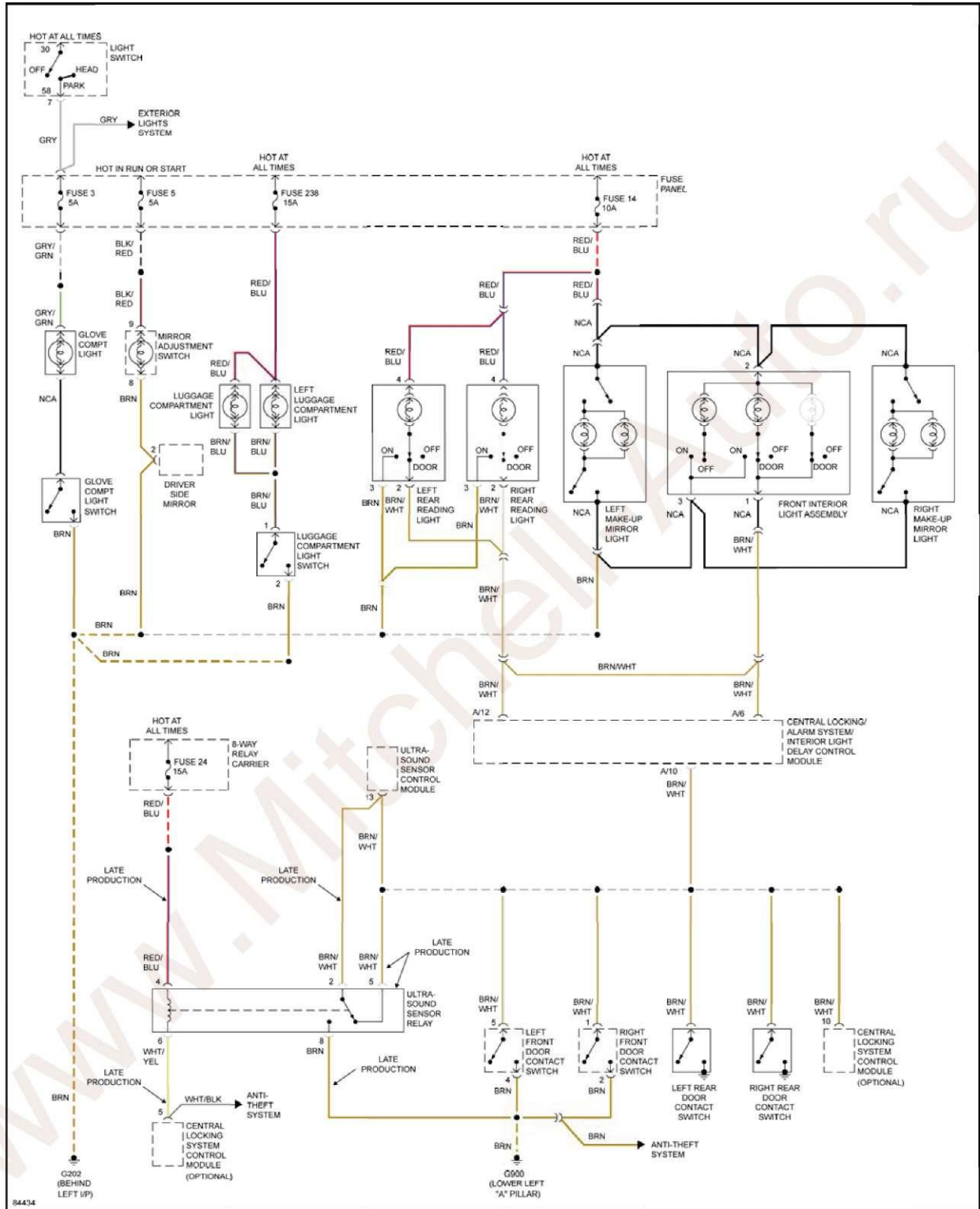


Fig. 21: Courtesy Lamps Circuit



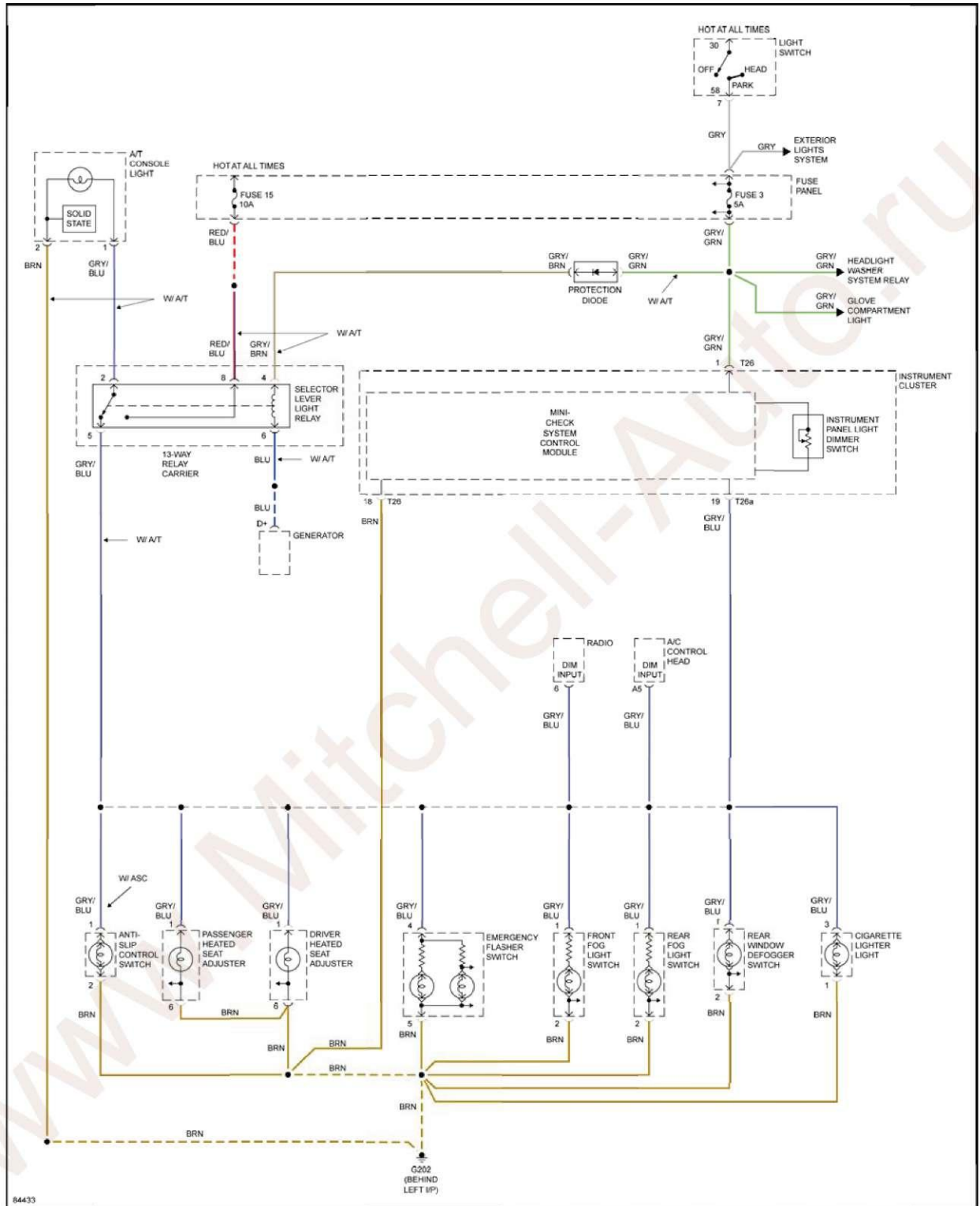


Fig. 22: Instrument Illumination Circuit

**POWER DISTRIBUTION**

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

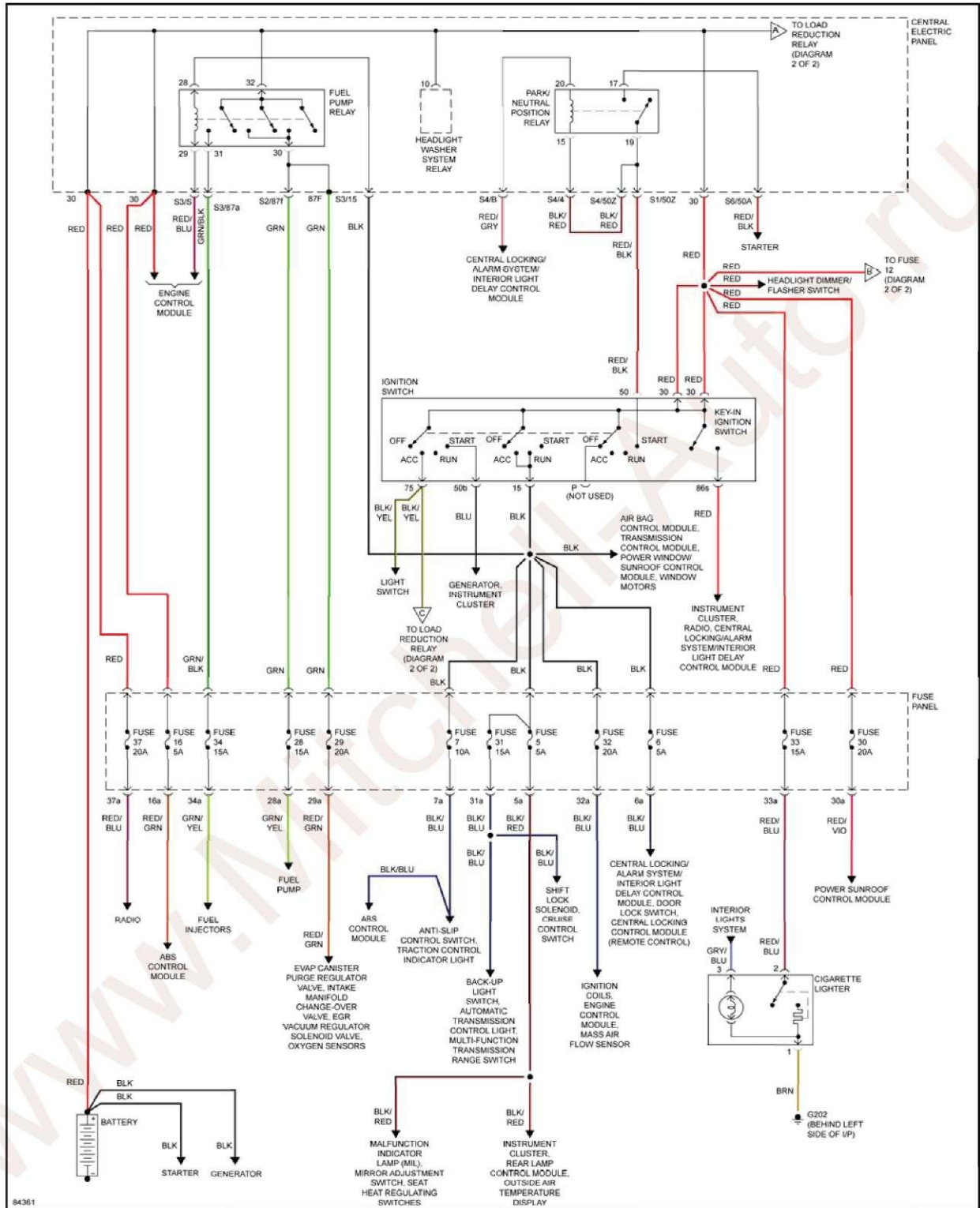


Fig. 23: Power Distribution Circuit (1 of 2)




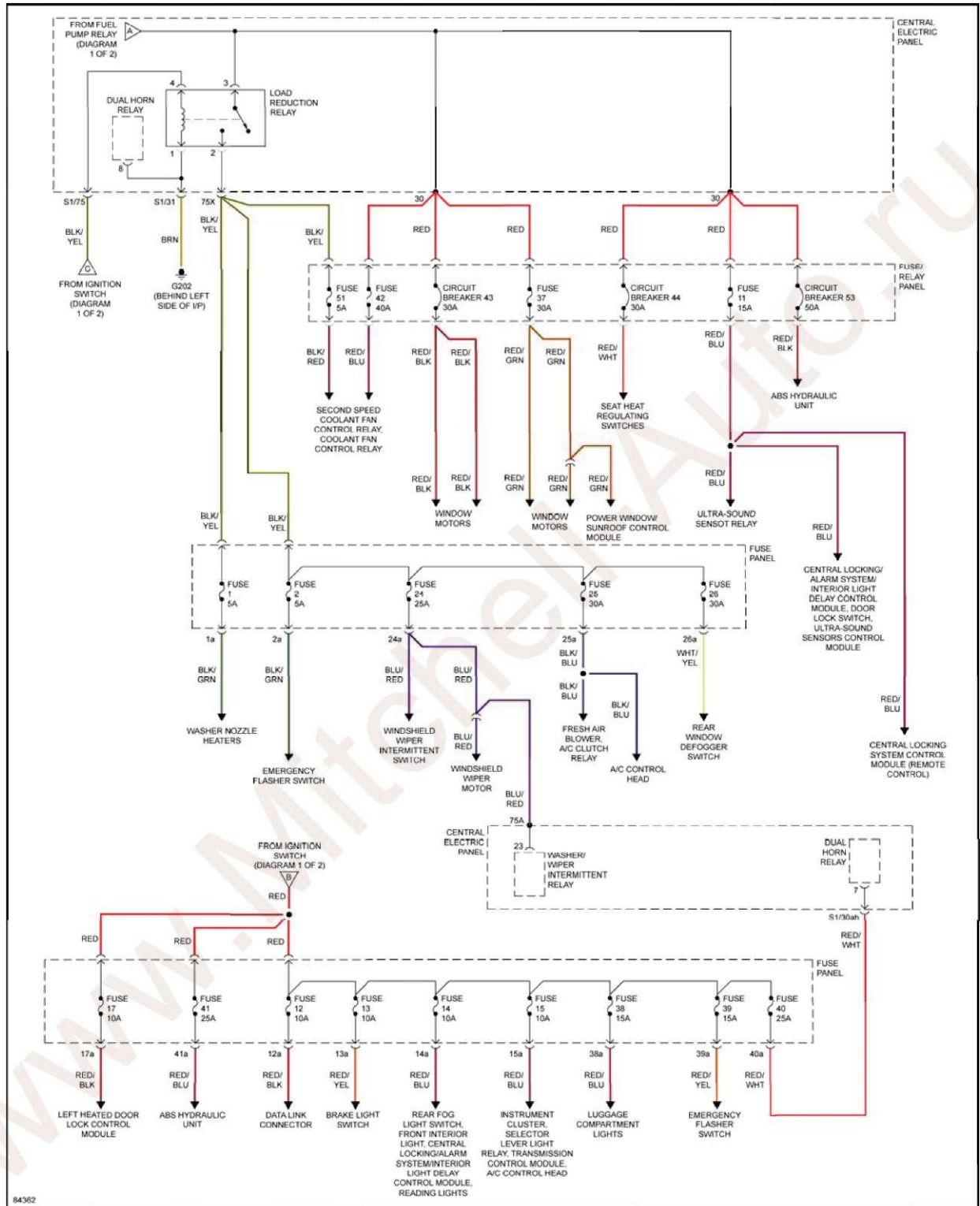


Fig. 24: Power Distribution Circuit (2 of 2)

POWER DOOR LOCKS

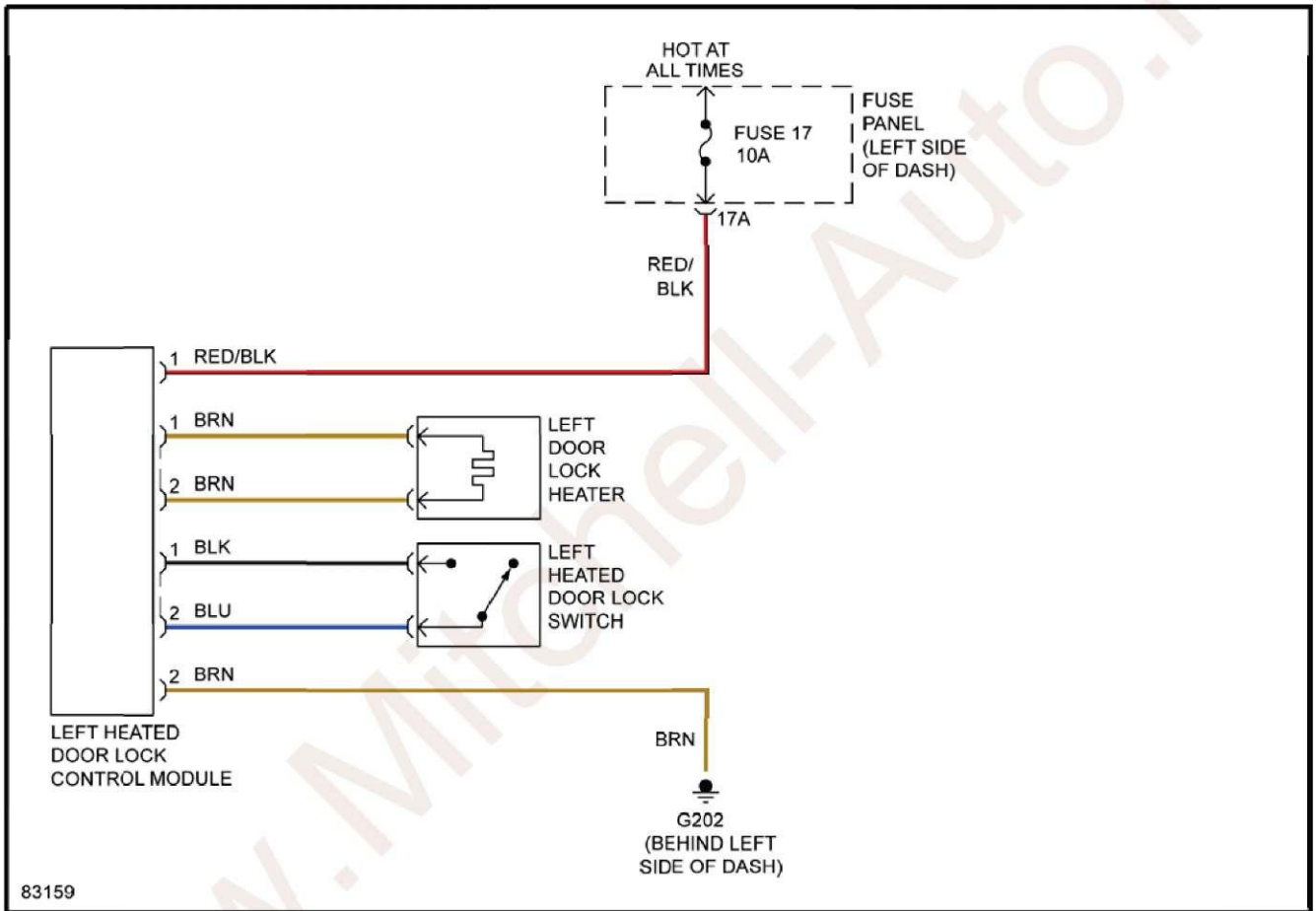

**Fig. 25: Heated Door Locks Circuit**

**POWER MIRRORS**

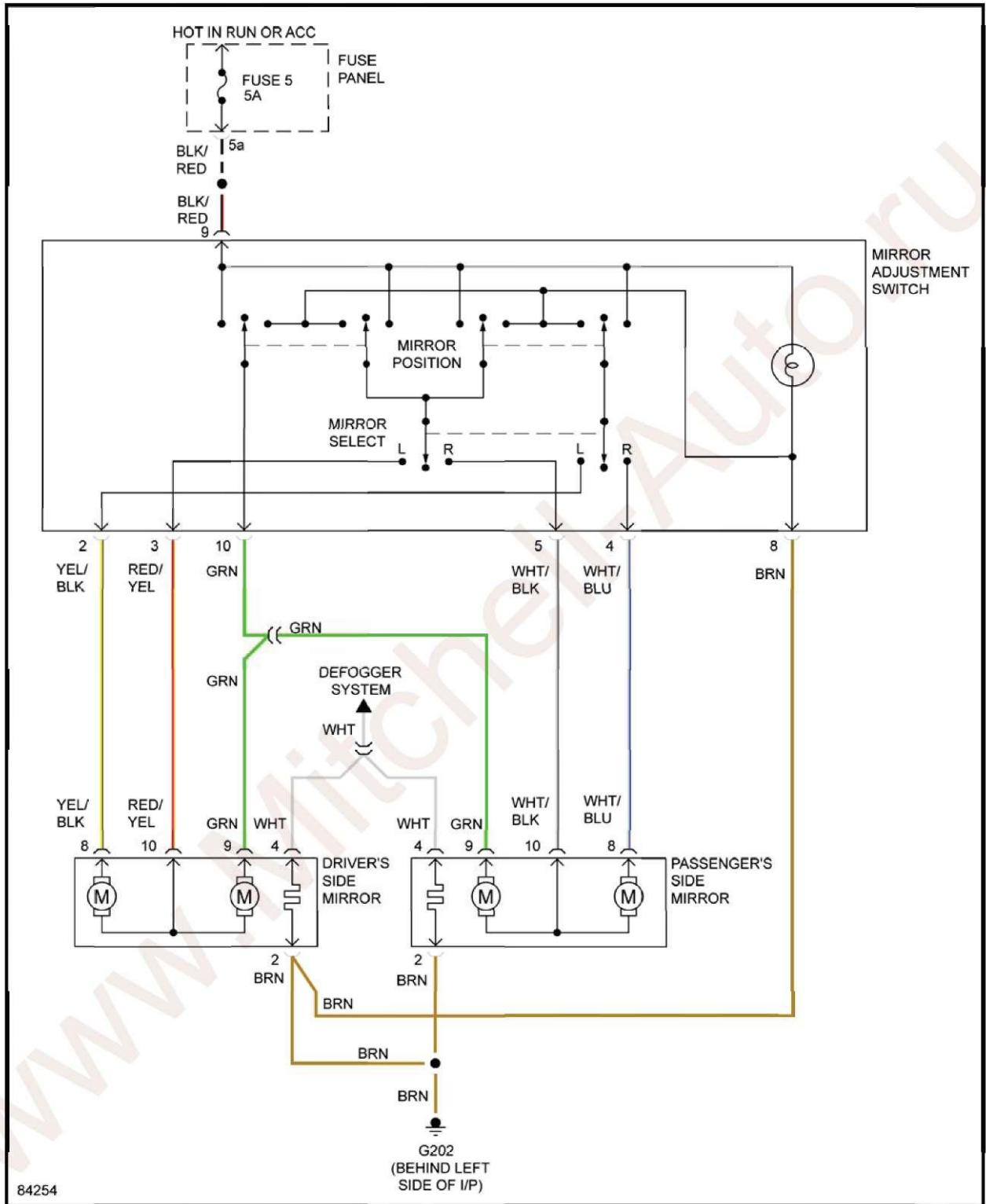


Fig. 26: Power Mirrors Circuit

**POWER SEATS**

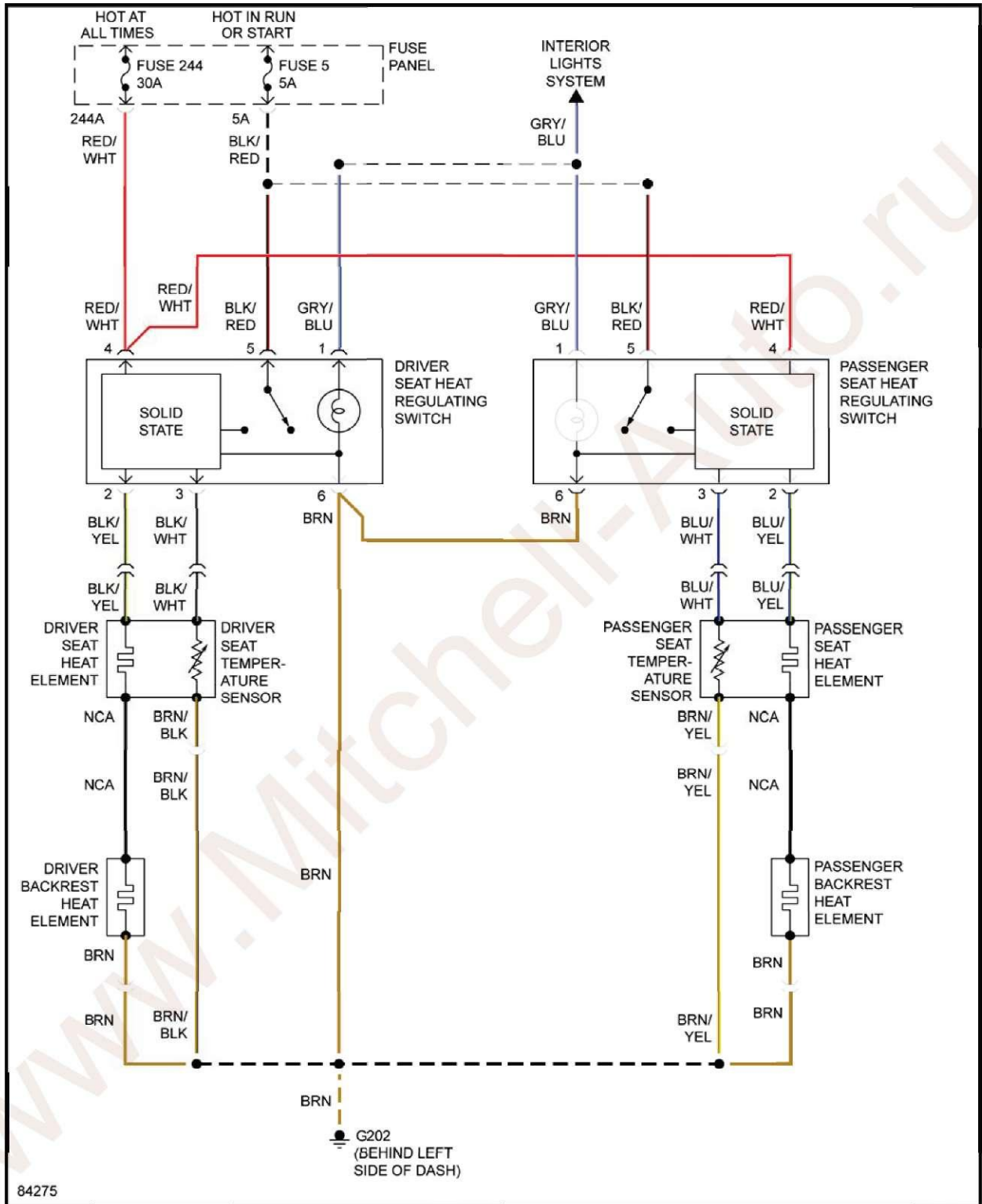


Fig. 27: Heated Seats Circuit

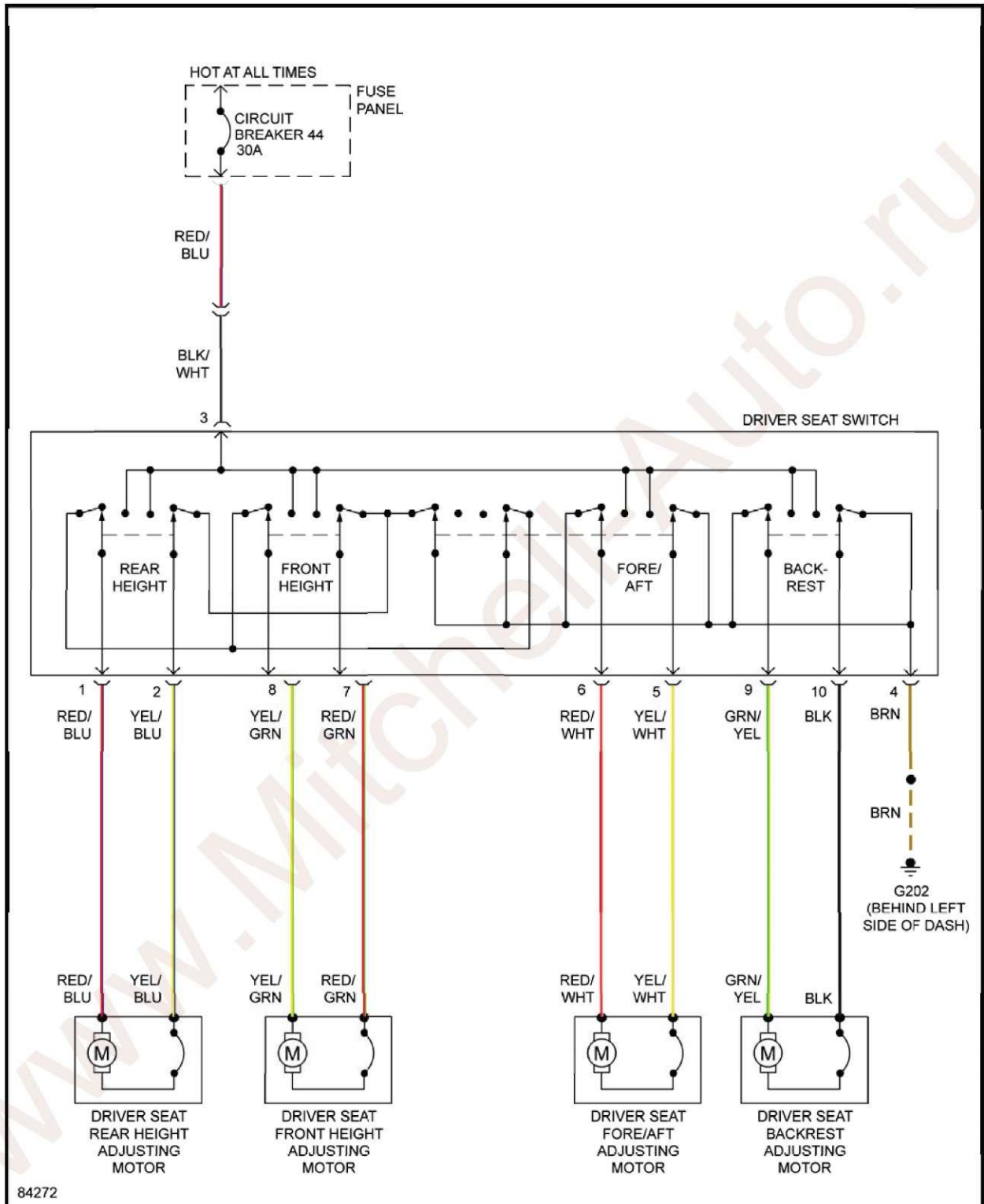


Fig. 28: Left Power Seat Circuit

POWER TOP/SUNROOF

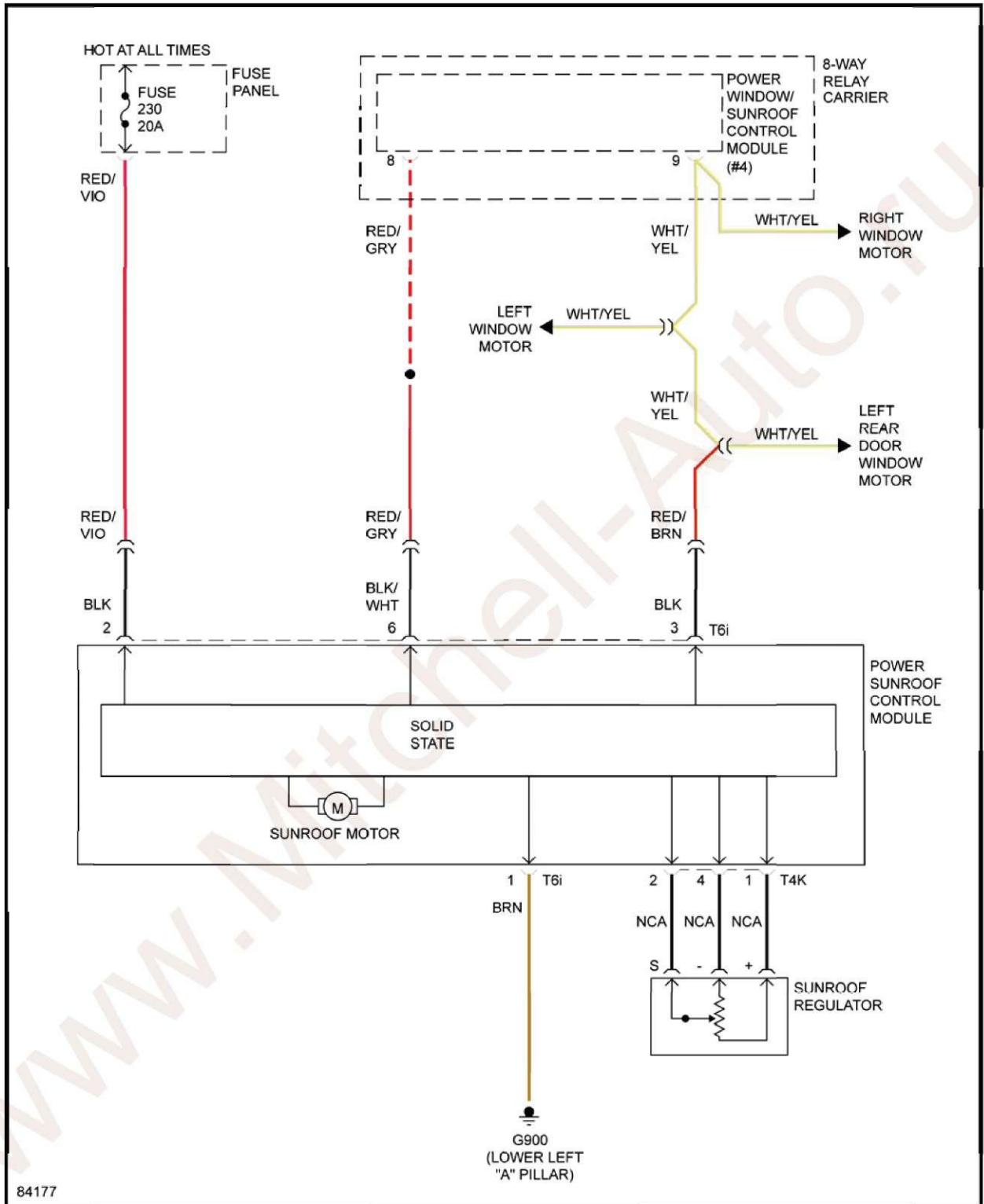


Fig. 29: Sunroof Circuit

POWER WINDOWS



# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

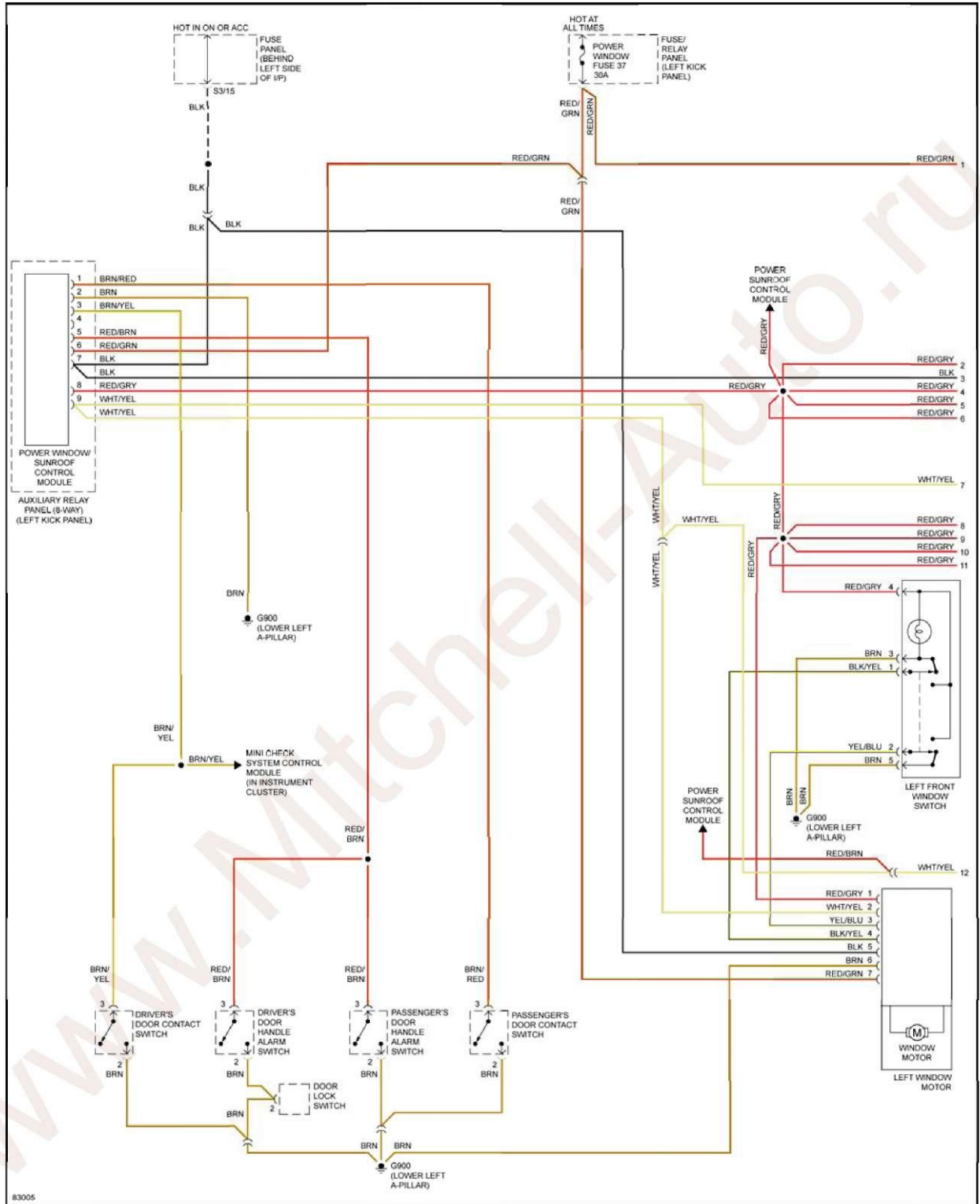


Fig. 30: Power Windows Circuit (1 of 2)



# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

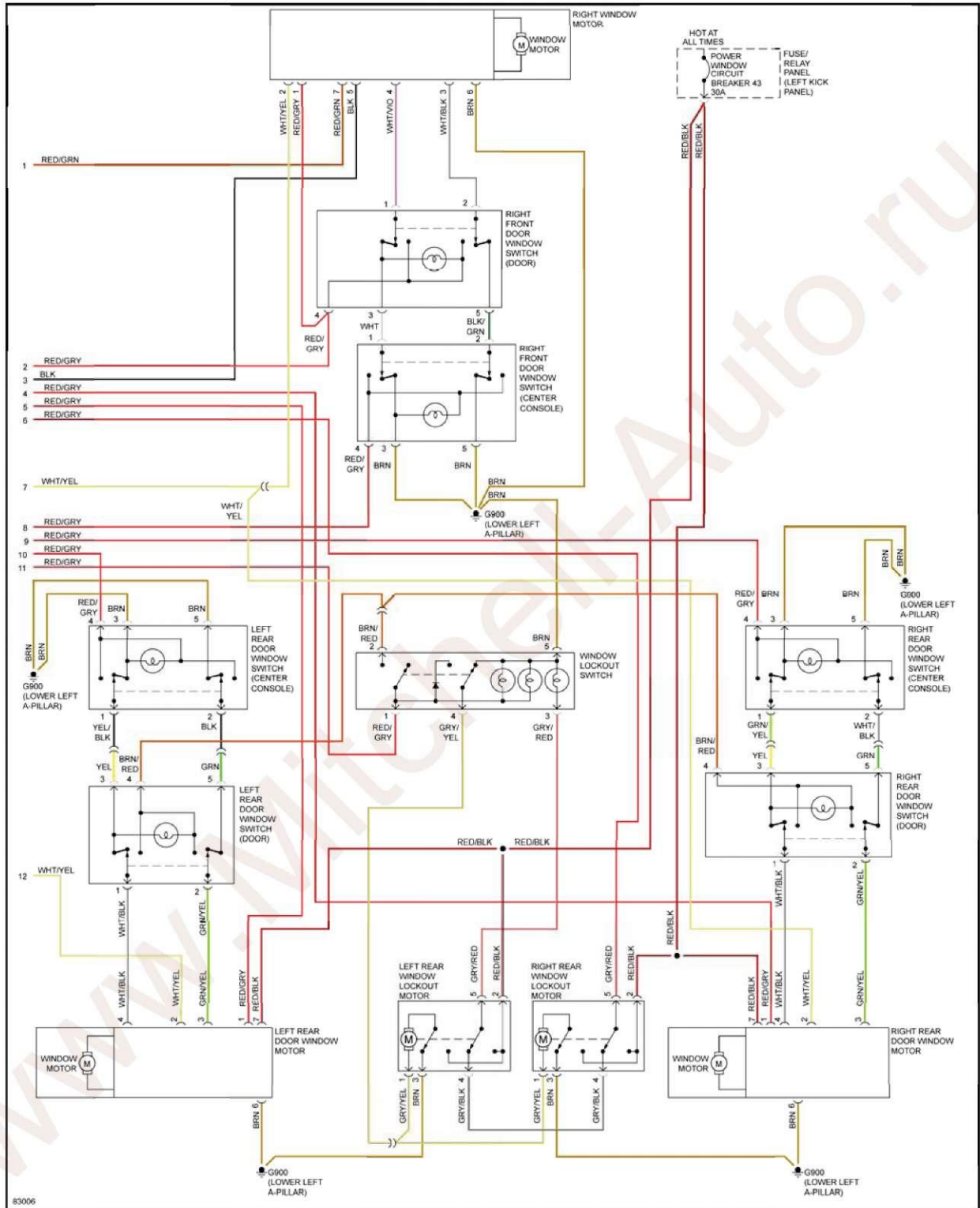


Fig. 31: Power Windows Circuit (2 of 2)

### RADIO

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

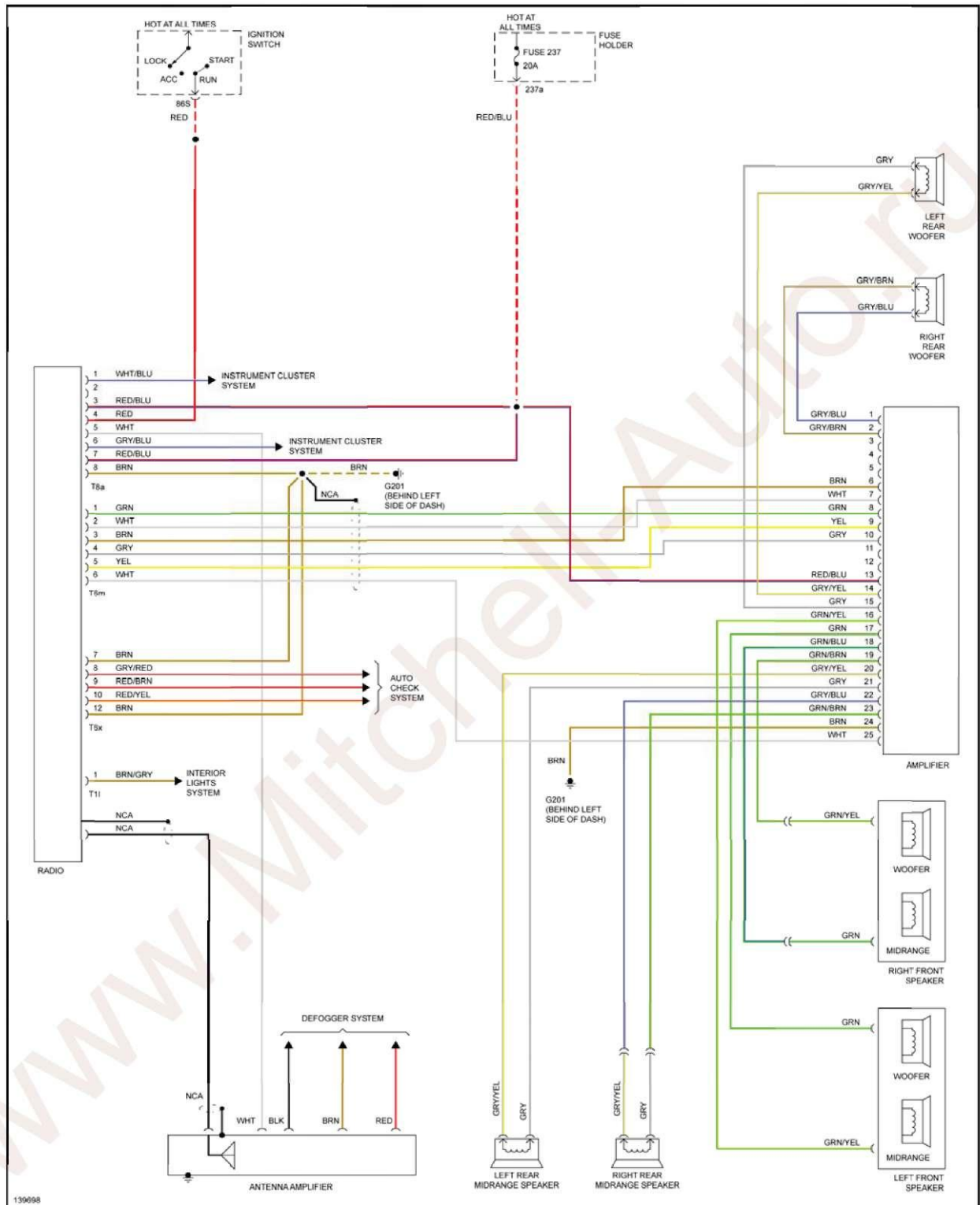


Fig. 32: Radio Circuit

## SHIFT INTERLOCK

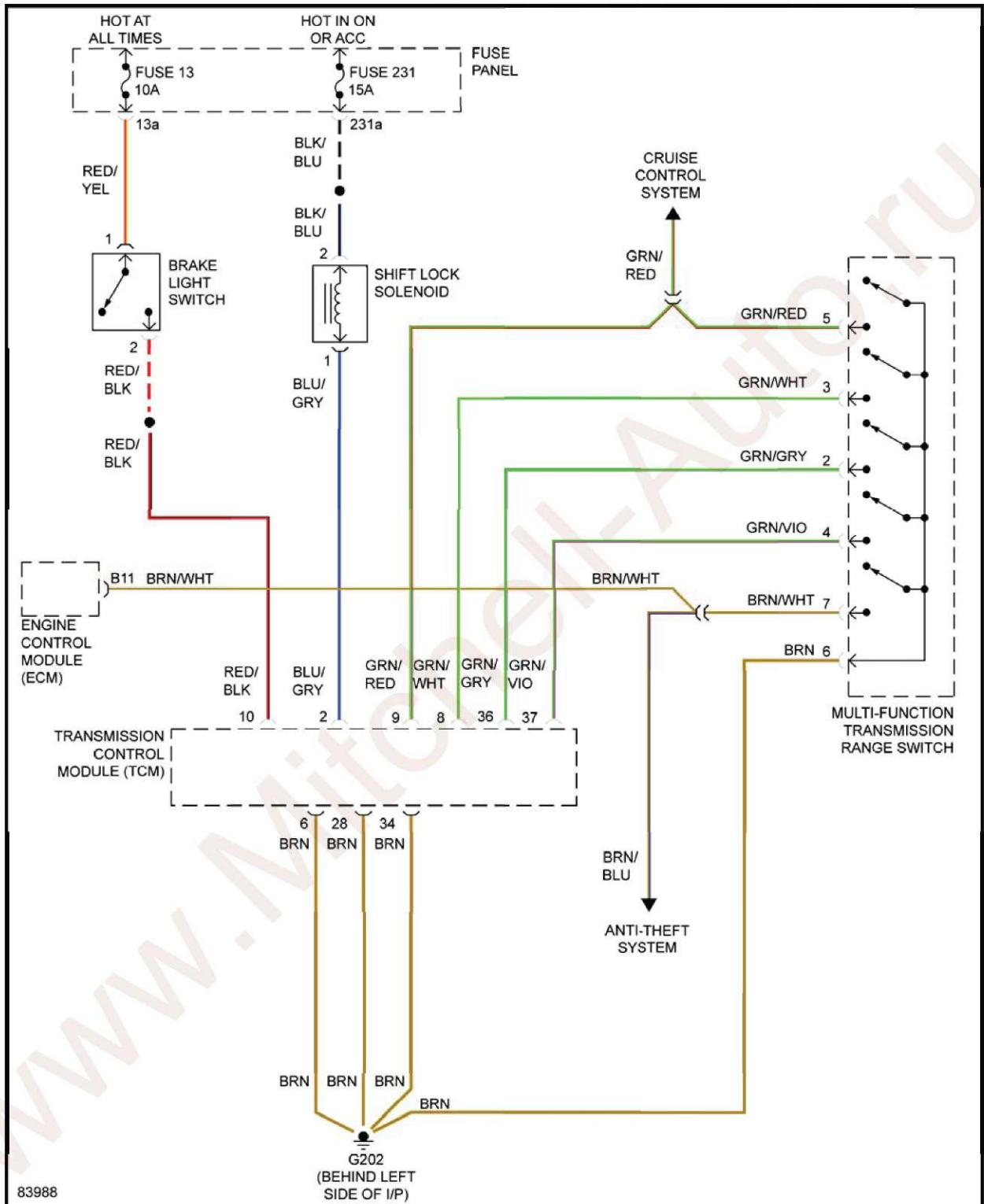


Fig. 33: Shift Interlock Circuit

STARTING/CHARGING

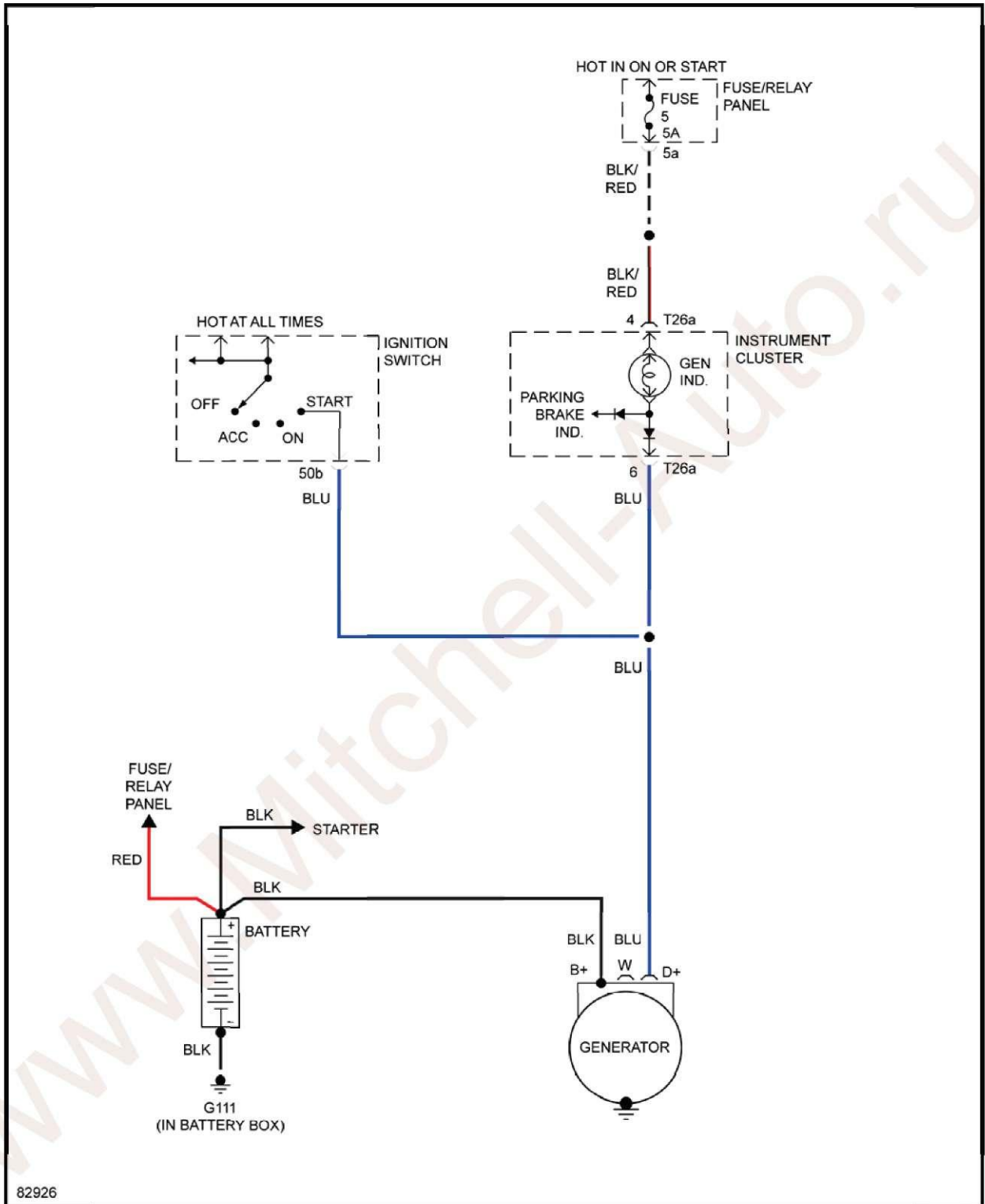


Fig. 34: Charging Circuit

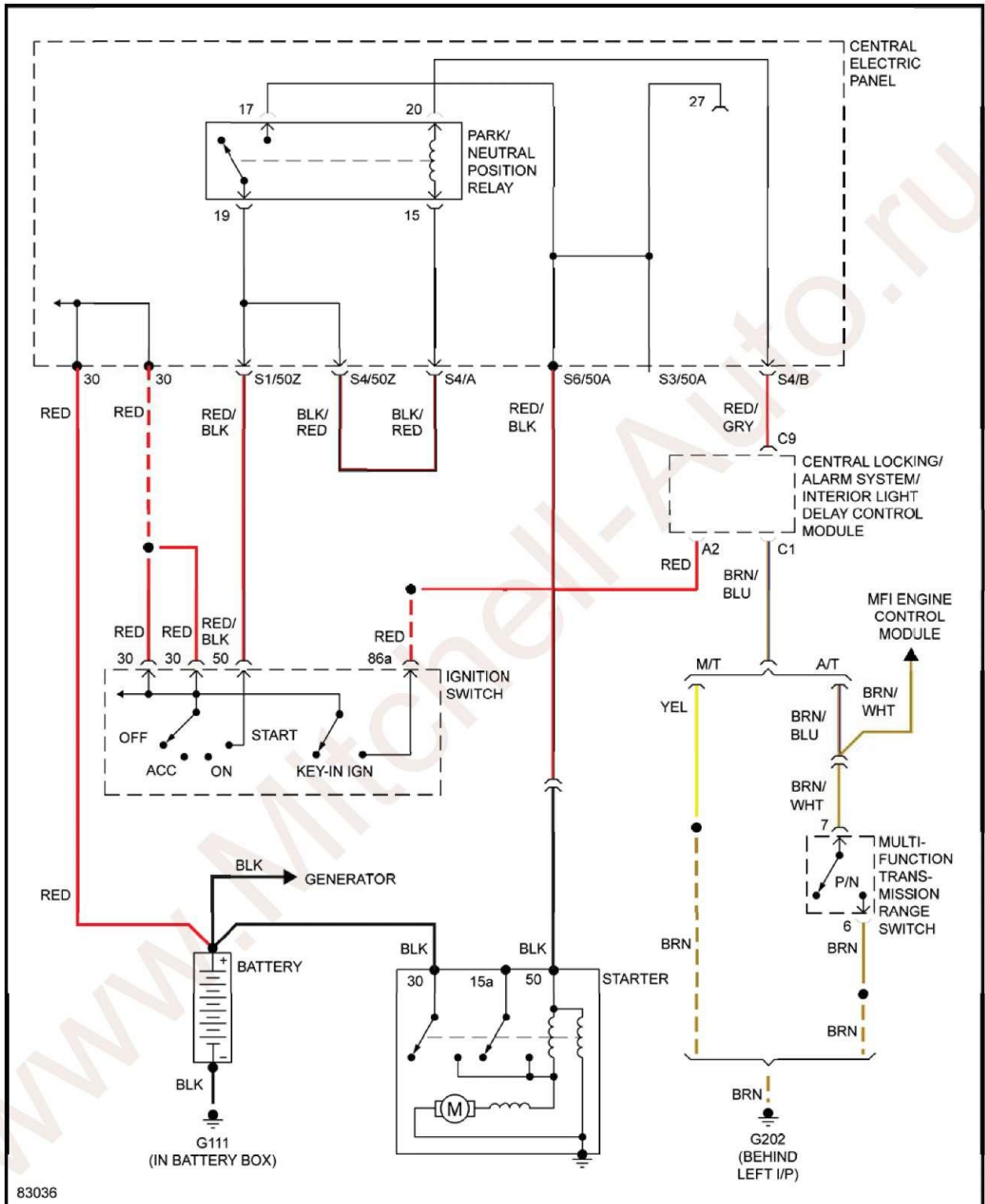


Fig. 35: Starting Circuit

SUPPLEMENTAL RESTRAINTS



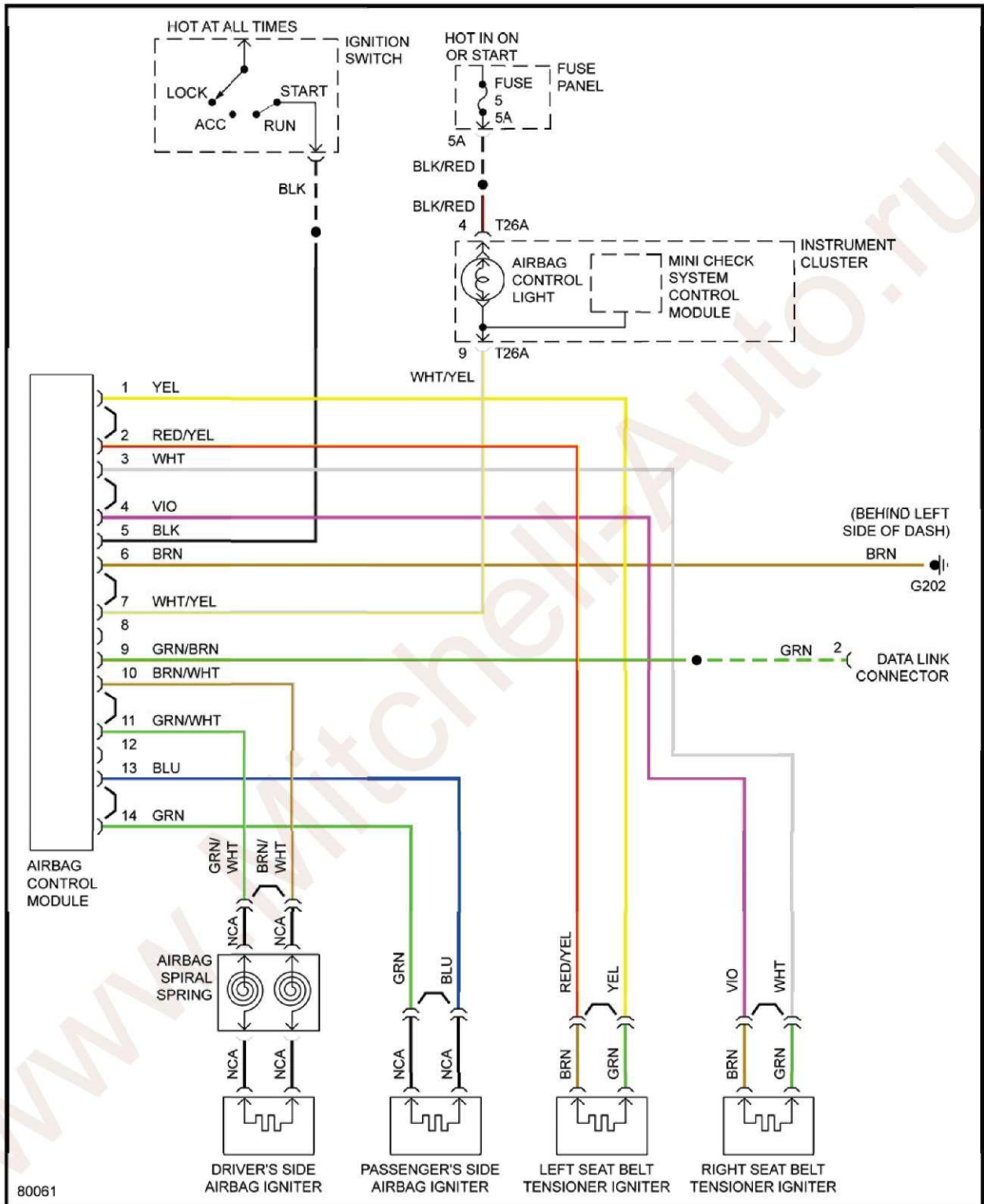


Fig. 36: Supplemental Restraints Circuit

## TRANSMISSION

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

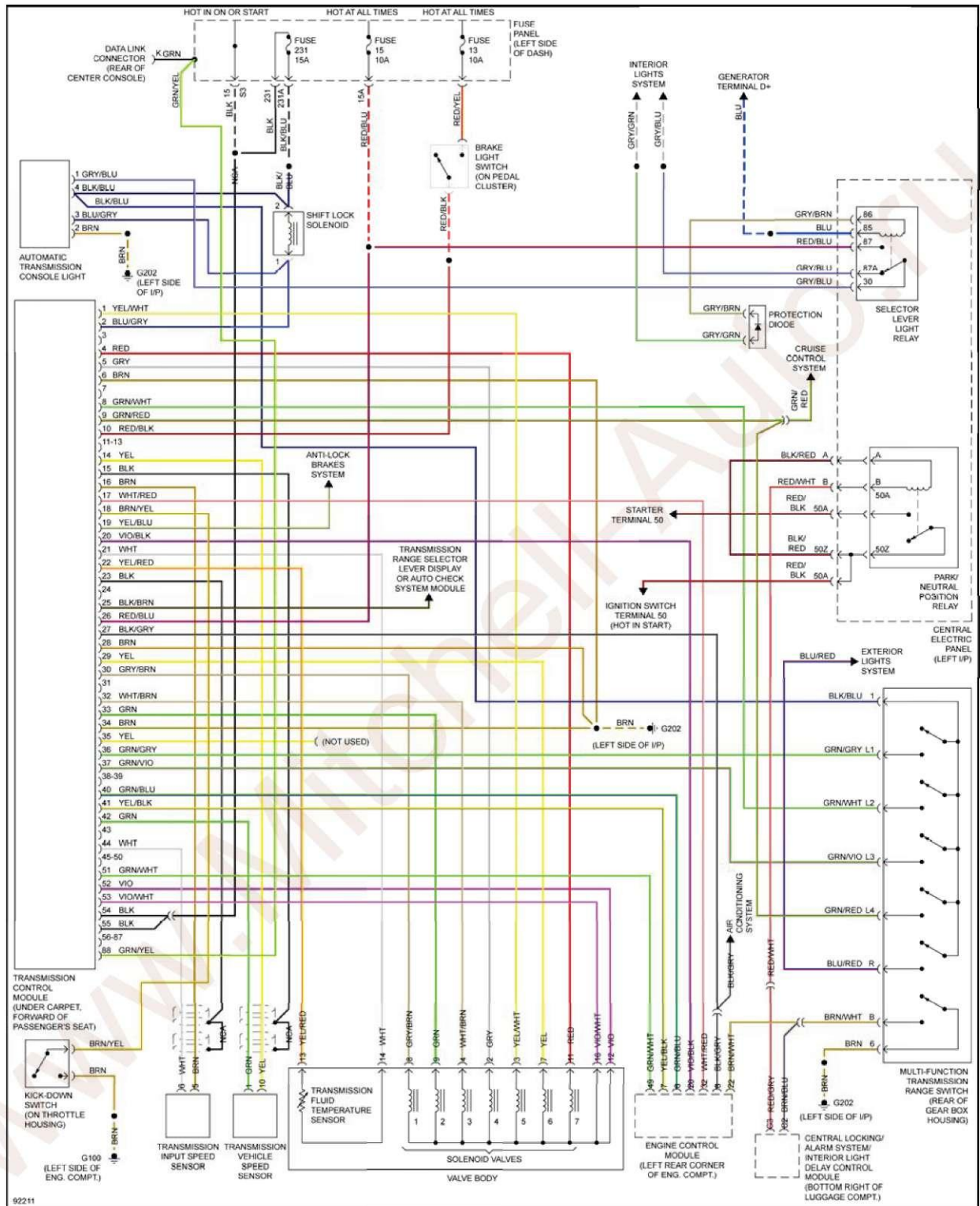


Fig. 37: A/T Circuit

## WARNING SYSTEMS

# 1996 Audi A4

## SYSTEM WIRING DIAGRAMS Audi - A4

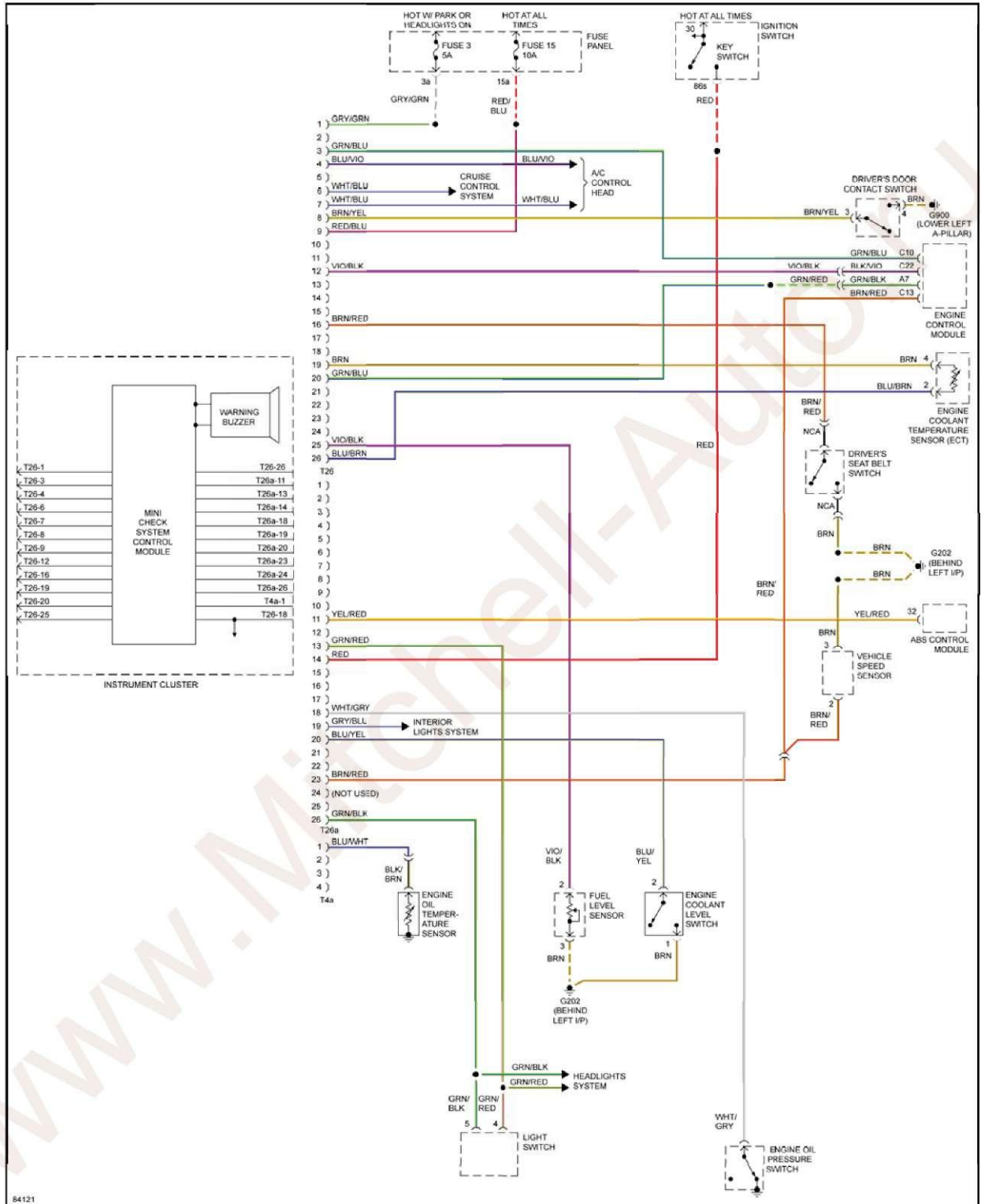


Fig. 38: Warning Systems Circuit

### WIPER/WASHER

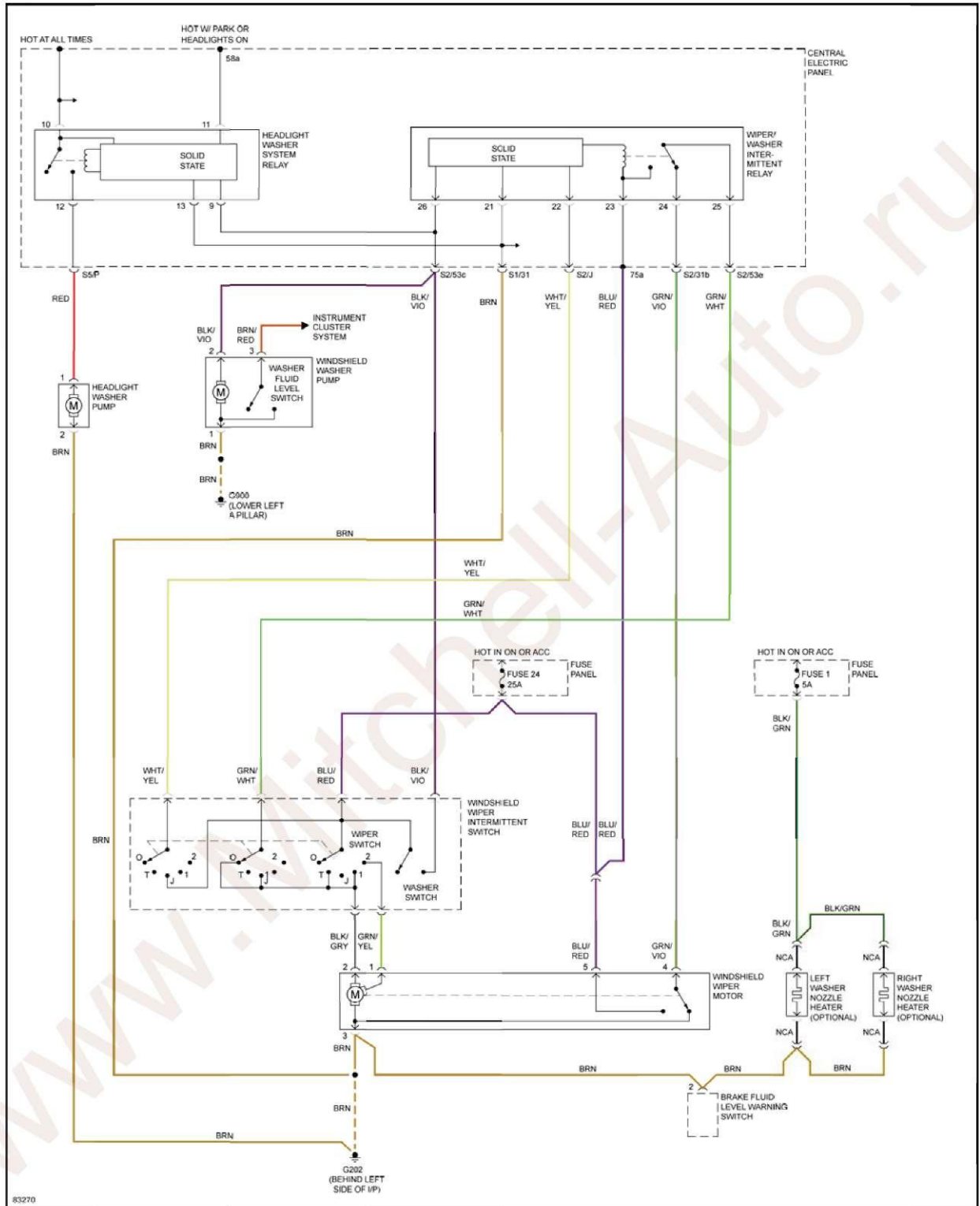


Fig. 39: Wiper/Washer Circuit

